

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 2301**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B.Tech****(SEM I) ODD SEMESTER THEORY EXAMINATION 2009-10  
ELECTRICAL ENGINEERING**


Time : 3 Hours]

[Total Marks : 100

**SECTION - A**1 Attempt all parts of the following :  $10 \times 2 = 20$ 

(Fill in the blanks/choose/match)

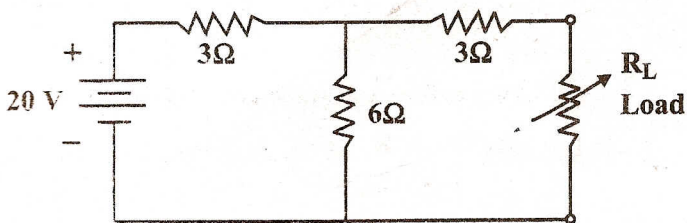- (i) The maximum power that can be supplied to the load in the following circuit is



- (a) 10 W  
(b) 20 W  
(c) 30 W  
(d) 40 W



- (ii) The coupling between two magnetically coupled coils is said to be the ideal if the coefficient of coupling is
- Zero
  - 0.5
  - 0.75
  - 1
- (iii) A sinusoidal current having rms value of  $8 \angle 0^\circ$  A is added to another sinusoidal current of rms value  $6 \angle 90^\circ$  A. The rms value of the resultant current is \_\_\_\_\_
- (iv) Which of the following conditions is common to both series and parallel resonance?
- current is maximum
  - power is low
  - impedance is minimum
  - power factor is unity
- (v) Which of the following formulae is used to express active power in a balanced three-phase circuit?
- $V_L I_L \cos \phi$
  - $\sqrt{3} V_L I_L \cos \phi$
  - $V_{ph} I_{ph} \cos \phi$
  - $\sqrt{3} V_{ph} I_{ph} \cos \phi$



- (vi) A moving coil instrument gives full scale deflection with 20 mA. The resistance of coil is 4 ohm. The value of series resistance needed for the instrument to read upto 30 V is \_\_\_\_\_.
- (vii) A 100 kVA single phase transformer operating at 0.9 power factor has 90% maximum efficiency. The iron loss will be \_\_\_\_\_.
- (viii) A 4-pole lap wound dc generator generates 200 V at 1000 rpm. If this generator is now wave wound and runs at 500 rpm, the generated voltage will be \_\_\_\_\_.
- (ix) A 3-phase induction motor connected from a 3-phase, 50 Hz ac supply runs at 720 rpm and has 4% slip. The number of poles in the motor are :
- (a) 4  
 (b) 6  
 (c) 8  
 (d) 16
- (x) Match the following (marks will be awarded if all matching are correct) :


<b>Type of Motor</b>	<b>Application</b>
(i) dc series motor	(a) Centrifugal pumps
(ii) Synchronous motor	(b) Cranes
(iii) 3-phase squirrel cage induction motor	(c) Hair dryer
(iv) Single phase shaded pole motor	(d) Condenser




## SECTION - B

2 Attempt any three parts of the following :  $10 \times 3 = 30$

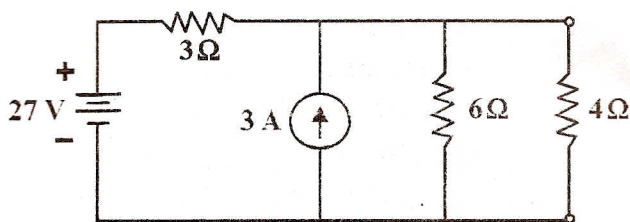- (a) (i) Determine current in 4 ohm resistance using Thevenin's theorem in the following circuit :



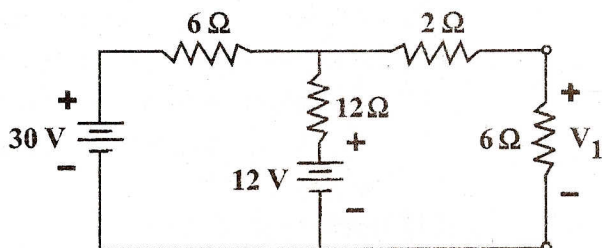- (ii) Find voltage  $V_1$  across 6 ohm resistance in the following circuit using loop analysis method :



- (b) A coil having a resistance of 6 ohm and an inductance of 0.0255 H is connected across a 230 V, 50 Hz ac supply. Calculate
- (i) current
  - (ii) power factor
  - (iii) active power



- (iv) reactive power
  - (v) apparent power
  - (vi) It is desired to improve power factor to 0.8. What value of capacitance to be connected in series R and what is reduction in reactive power?
- (c) A balanced star connected inductive load is connected to a 400 V, 50 Hz ac supply. Two wattmeters used to measure supply power indicate 8000 W and 4000 W respectively. Determine
- (i) line current
  - (ii) impedance of each phase
  - (iii) resistance and inductance of each phase.
- (d) A 20 kVA, 2000 V/200 V, single phase 50 Hz transformer has a primary resistance of 1.5 ohm and a reactance of 2 ohm. The secondary resistance and reactance are 0.015 ohm and 0.02 ohm respectively. The no load current of transformer is 1 A at 0.2 power factor. Determine
- (i) equivalent resistance, reactance and impedance referred to primary
  - (ii) supply current
  - (iii) total copper loss.
- Draw approximate equivalent circuit.
- (e) A dc shunt generator delivers 50 kW at 250 V when running at 500 r.p.m. The armature and field resistances are 0.05 ohm and 125 ohm respectively. Calculate the speed of the same machine and developed torque when running as a shunt motor and taking 50 kW at 250 V. Allow 1 volt per brush for contact drop.



## SECTION - C

**Note :** Attempt all questions of this section. **10×5=50**

- 3 Attempt any two parts of the following :
- State and explain superposition theorem.
  - Discuss different types of voltage and current sources.
  - Explain star-delta transformation.
- 4 Attempt any two parts of the following :
- Explain parallel resonance and draw graphs of  $\alpha$ ,  $\beta$  and  $\gamma$  against frequency.
  - What is meant by power factor? What is its significance? How will you obtain power factor from kVA triangle?
  - For two phasors  $A = a_1 + jb_1$  and  $B = a_2 - jb_2$ , obtain their multiplication and division using polar form of representation.
- 5 Explain construction and working principle of a single phase induction type energy meter. How is energy measured?

**OR**

What is a three phase system? Give its necessity and advantages. What is meaning of phase sequence and how can it be changed?



- 6 Attempt any two parts of the following :
- (a) Draw and explain hysteresis loop. What is its significance?
  - (b) Explain single phase autotransformer and give its application.
  - (c) Derive e.m.f. equation of a single phase transformer and obtain relation for secondary to primary winding voltages.
- 7 Attempt any two parts of the following :
- (a) Derive an equation for generated torque in dc motor.
  - (b) Draw slip-torque characteristics of a three phase induction motor and explain its various regions of operation.
  - (c) Explain principle of operation of a synchronous motor and give its applications.
-