



Printed Pages : 3

TEC101

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3033

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech

(SEM I) ODD SEMESTER THEORY EXAMINATION 2009-10
ELECTRONICS ENGINEERING

Time : 3 Hours]

[Total Marks : 100

Note : Attempt all the questions.


1 Attempt any two parts of the following : $10 \times 2 = 20$

- (a) With a neat energy band diagram, explain the working of a p-n junction diode in reverse bias.
- (b) Draw the forward characteristics of a p-n junction diode and explain its :
 - (i) static resistance
 - (ii) dynamic resistance and
 - (iii) average a.c. resistance.
- (c) Name the capacitances associated with a p-n junction diode and explain the causes and dependence of these capacitances.



2 Attempt any two parts of the following : $10 \times 2 = 20$

 (a) Explain the working of following circuit :



(b) Draw the circuit of a full wave rectifier. Derive the expression for its ripple factor.

(c) Draw the output waveform of a full wave rectifier and compare its performance with (i) C filter (ii) LC filter.

3 Attempt any two parts of the following : $10 \times 2 = 20$

(a) Draw the BJT circuits for CB, CC and CE configurations. Compare Z_i , Z_o , A_V and A_I for the above configurations.

(b) Draw the circuit of a BJT in CE configuration employing voltage divider biasing. Calculate its stability against I_{CO} .

(c) Using a low frequency hybrid model, calculate A_V and A_I of a 2 stage RC coupled BJT amplifier.



Attempt any **two** parts of the following : $10 \times 2 = 20$

- (a) With a neat sketch, explain the working of an n-channel JFET.
- (b) With a neat sketch, explain the working of a p-channel depletion mode MOSFET.
- (c) Draw the circuit of a JFET amplifier in all the three configurations. Compare A_V , A_I , Z_i , Z_o for all of them.

Attempt any **two** parts of the following : $10 \times 2 = 20$

- (a) (i) Convert

$FE \phi A_{\text{hex}}$ into Decimal 7650 octal into hex 11010110 binary into octal.

- (ii) Draw the circuit of a 2 input EX-OR gate using four 2 input NAND gates.

- (b) Minimise the following K-Map :

	CD	00	01	11	10
AB					
00				1	
01		1	1	1	
11			1	1	1
10			1		

- (c) Draw an op-amp based circuit to give $V_0 = V_1 + V_2 + V_3$.

