

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 1116

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B. Tech.

(Semester-I) Theory Examination, 2012-13

ELECTRONICS ENGINEERING

Time : 3 Hours]

[Total Marks : 100

Note : Attempt questions from each Section as per instruction.

Section-A

Attempt *all* parts of this question. Each part carries 2 marks. $2 \times 10 = 20$

1. (a) If a pure silicon crystal has 1 million free electrons inside it, how many holes does it have? What happens to the number of free electrons and holes, if the ambient temperature increases?
- (b) Define the use of Surge resistor.
- (c) Draw the schematic of Peak-to-Peak detector.
- (d) How is Varactor used?

(e) Calculate the output voltage appear across R_{load} (in Fig. 1).

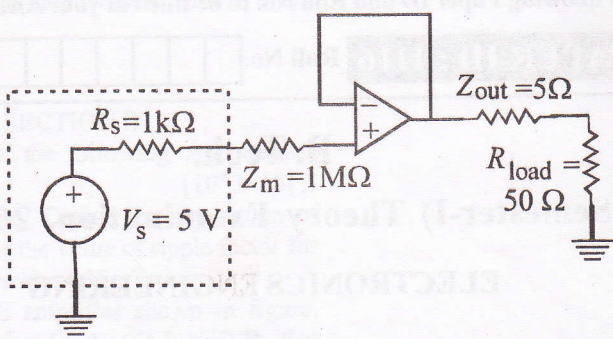


Fig. 1

(f) Find resistance R_b in Fig. 2 to bring transistor to threshold of saturation $V_{CB} = 0$, $V_{BE} = 0.7$ V, $\alpha = 0.96$.

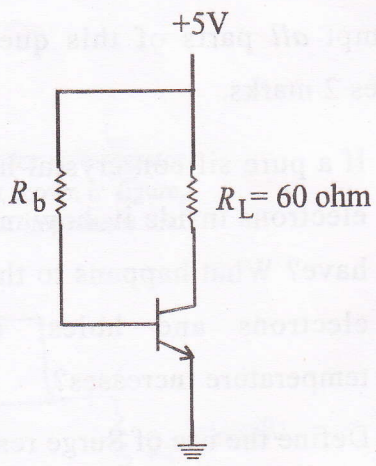


Fig. 2

2. A
cr
(a) W
ri
hu
(b) F
C
A

(c) D
w
fr
∞



- (g) MOSFET
- (h) List the primary differences between JFET and MOSFET.
- (i) How to test probes using CRO?
- (j) List the four specifications of DC power supply.

Section-B

Attempt any *three* parts of this question. Each part carries 10 marks. $10 \times 3 = 30$

2. (a) (i) Sketch and explain the circuits of a combination clipper which limit the output between $\pm 10V$. Assume the diode voltage is $0.7V$.
- (ii) With neat diagram and waveforms explain the working of a negative clamper and also write the condition for stiff clamper.
- (b) Given $\beta = 50$ for the transistor circuit shown in Fig. 3, find the transistor currents I_C , I_E and I_B . In which region is the transistor operating? Justify.

(i)
(j)

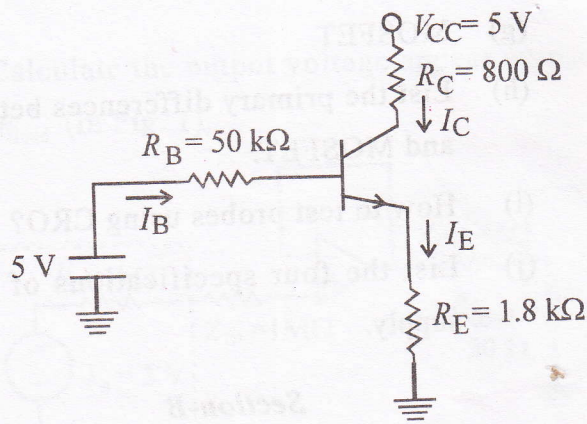


Fig. 3

2. A
ca
(a) W
rij
ha
(b) Fc
C:
A:

(c) Describe the drain curves and transconductance curve of enhancement mode and depletion mode MOSFET. Derive an expression for g_m of JFET configuration.

(d) Draw the block diagrams of four types of Negative Feedback Amplifiers. Also calculate VCVS voltage gain, input impedance and output impedance.

(e) (i) Explain, how you would measure phase of signal from C.R.O.

(ii) Describe the working of digital multi-meter with neat block diagram.



(c) Dr
wi
fin
col



Section-C

Attempt *all* questions of this Section. Each question carries 10 marks. $10 \times 5 = 50$

3. Attempt any two parts :

(a) Sketch the waveform output V_{out} in the circuit of Fig. 4, indicating the values of maximum positive and negative output voltages.

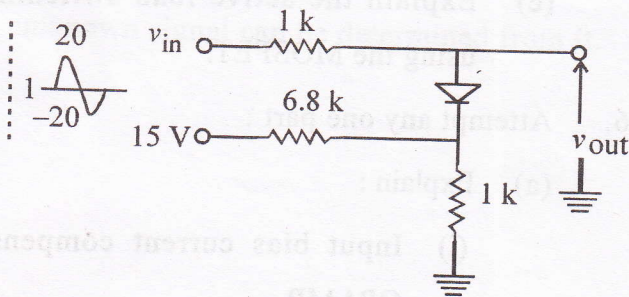


Fig. 4

- (b) Explain the working of Voltage Multiplier.
- (c) Explain the working of Schottky diode.

4. Attempt any two parts :

(a) Explain the working of an emitter follower circuit with its circuit diagram.

- (i) (b) Draw the schematic of direct couple output stage and explain its working.
- (ii) (c) Compare different types of biasing methods.

5. Attempt any two parts :

- (a) Define Ohmic region, gate cut-off voltage and transconductance in JFET.
- (b) Draw the schematic of CS JFET amplifier and determine A_v .
- (c) Explain the active load switching circuit using the MOSFET.

6. Attempt any one part :


- (a) Explain :
 - (i) Input bias current compensation in OPAMP.
 - (ii) Integrator using OPAMP.
 - (iii) Zero crossing detector using OPAMP.
- (b) (i) Obtain an expression for the closed loop gain of a non-inverting amplifier.
- (ii) Describe the method of measuring and calculating CMMR of an OPAMP.

(c) Draw with find com



7. Attempt any two parts :

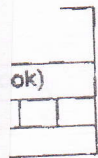- (a) Compare the design issues of analog meters and digital meters.
- (b) Draw the basic block diagram of a function generator and explain the function of each block.
- (c) Explain the procedure to obtain the Lissajous pattern on the screen of a CRO and also explain how the phase of an unknown signal can be determined from it.



of
le
ne
be
or
V-
ith
lar
the
ype