



Printed Pages : 7

TEC-201/101

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3034Roll No. **B. Tech.****(SEM. II) EXAMINATION, 2007-08****ELECTRONIC ENGINEERING***Time : 3 Hours]**[Total Marks : 100*

- Note :**
- (1) Attempt **all** questions.
 - (2) All question carry **equal** marks.
 - (3) In case of numerical problems assume data whenever not provided.
 - (4) Be precise in your answer.

1 Attempt any **four** parts : **5×4**

- (a) The mobility of free electrons and holes in pure germanium are 3800 and 1800 m² / Vs respectively. The corresponding values for pure silicon are 1300 and 500 m² / Vs respectively. Determine the values of intrinsic conductivity for both. Assume $n_i = 2.5 \times 10^{13} \text{ cm}^{-3}$ for germanium and $n_i 1 = 2.5 \times 10^{10} \text{ cm}^{-3}$ for silicon at room temperature.
- (b) Describe the difference between majority and minority carriers.
- (c) Define the static and dynamic resistance of the diode, how these resistances are measured.



- (d) Discuss the difference between diffusion and transition capacitances.
- (e) Draw the reverse characteristics of a diode; define avalanche and Zenor breakdown regions.
- (f) Define the reverse recovery time of a diode.

2 Attempt any four parts of the following : 5×4

- (a) Sketch V_o for the circuit shown in fig. 1 D1 and D2 are silicon diodes.

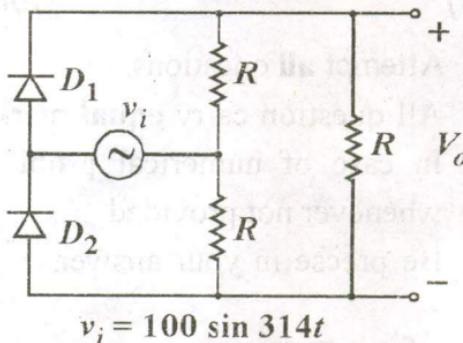


Fig. 1

- (b) For the circuit shown in fig. 2 sketch iR and V_o .
(D1 and D2 are Si diode.)

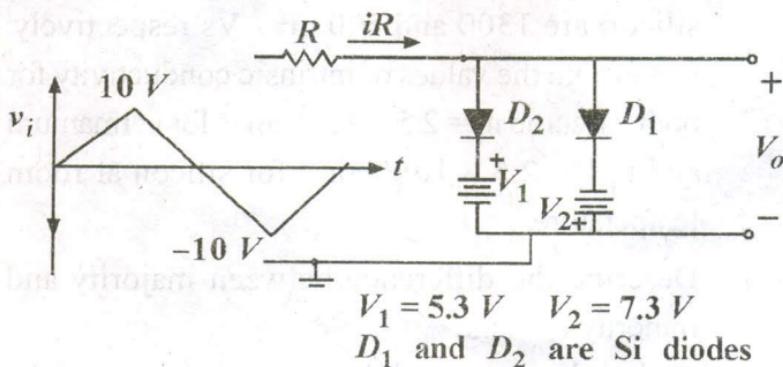


Fig. 2

- (c) Determine V_L , I_L , I_Z and I_R for the circuit R_L is 470 ohms.

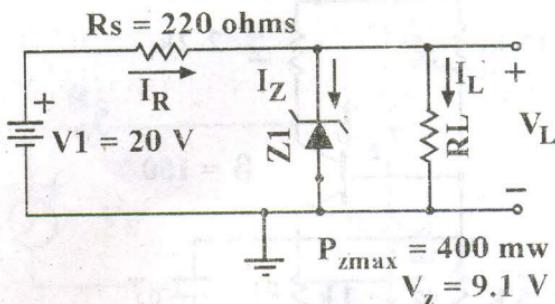


Fig. 3

- (d) For the clamping circuit shown in fig. 4 sketch for V_O .

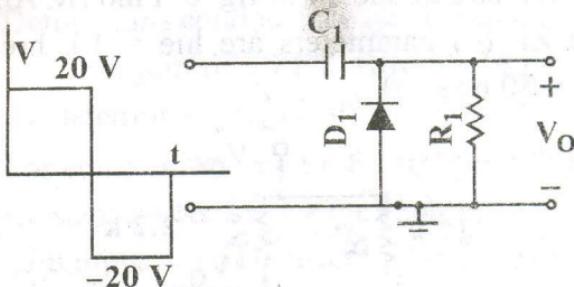


Fig. 4

- (e) Draw the circuit diagram of a bridge rectifier. Discuss the operation and find dc and rms output voltage.
 (f) With the help of the circuit diagram explain the working of a voltage doubler.

3 Attempt any two parts of the following : 10×2

- (a) For a voltage divider biasing circuit shown in fig. 5. Find I_C , V_{CE} , I_B , V_E and V_B .

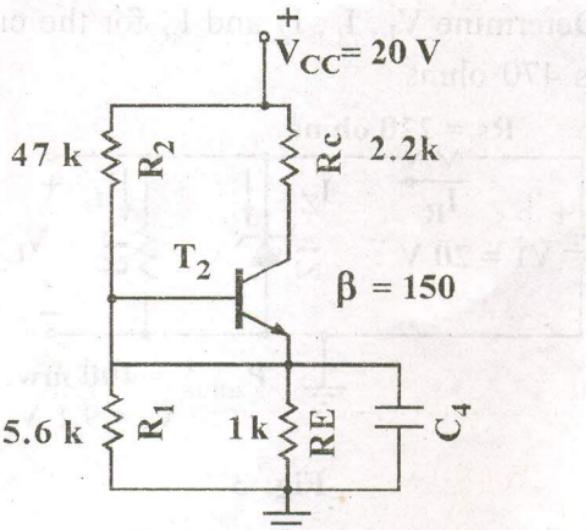


Fig. 5

- (b) For the circuit shown in fig. 6. Find A_v , A_i , Z_o and Z_i . (h) parameters are $h_{ie} = 1\text{ k}$ $h_{re} = 0$ $h_{fe} = 50$ $h_{oe} = 0$.

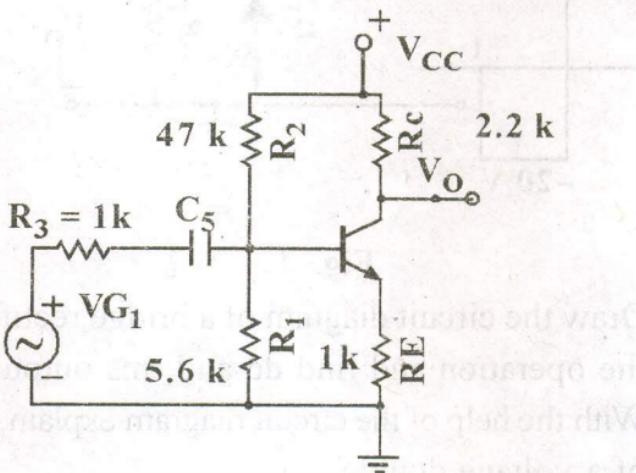


Fig. 6

- (c) Derive the expression for input impedance and voltage gain for a CE and shown in fig. 7 using simplified (approximate) equivalent circuit i.e. $h_{re} = h_{oe} = 0$.

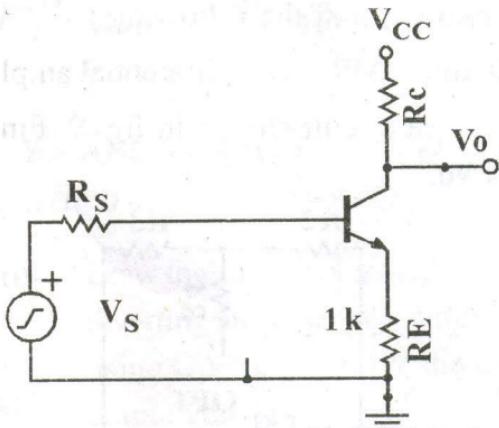


Fig. 7

4 Attempt any **two** parts of the following :

10×2

- Define trans conductance (gm) output resistance (r_p) and gain of a FET. How these parameters are determined graphically.
- For common source FET amplifier with source resistance is R_s . Derive the expression for voltage gain input impedance and output impedance.
- For a circuit shown in fig. 8. Calculate V_o , Z_i and Z_o . Input is $V_i = 0.2$ V (rms.)

$$I_{DSS} = 9 \text{ mA} \quad V_p = -4.5 \text{ V}$$

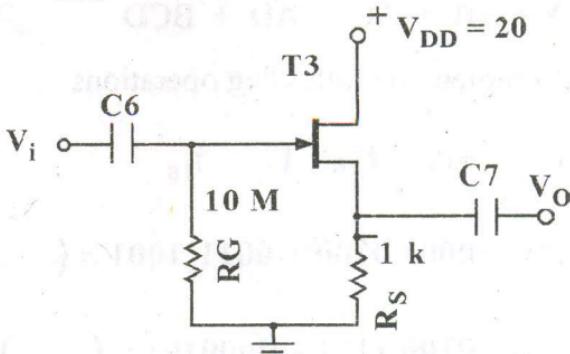


Fig. 8

5 Attempt any two parts of the following :

10×2

- (a) (i) Define CMRR of a differential amplifier.
(ii) For the circuit shown in fig. 9. Find out voltage, V_o .

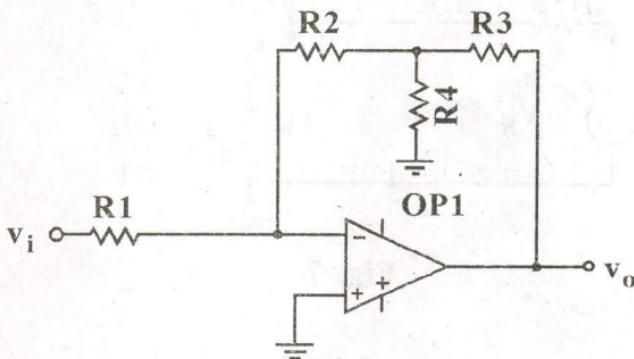


Fig. 9

- (b) (i) Convert the following numbers :

$$(1) \quad 2D6_{16} = (\quad)_2$$

$$(2) \quad 011010110_2 = (\quad)_{16}$$

- (ii) Convert the following function in to canonical forms :

$$Y = AB + AC + AD + BCD$$

- (iii) Complete the following operations :

$$(1) \quad 8_{16} + F_{16} = (\quad)_{16}$$

$$(2) \quad 0001\ 0100 + 0011\ 1001 = (\quad)_2$$

$$0100\ 1111 - 0000101 = (\quad)_2$$

- (iv) Minimize the following function using Boolean algebra.

$$Y = \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + AB\bar{C}\bar{D} + ABC\bar{D} + A\bar{B}CD + A\bar{B}\bar{C}D + A\bar{B}CD$$

- (c) (i) Draw the circuits of inverting amplifier, non-inverting amplifier and difference amplifier using Op-Amp. Derive the expression for output voltage.
- (ii) Draw the circuit of integrator and differentiate using Op-Amp, derive the expression for output.
-

