

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3302 Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(Second Semester) Theory Examination, 2010-11

ELECTRONICS ENGINEERING

Time : 3 Hours]

[Total Marks : 100

Note : Attempt all questions.

1. Attempt each of the following parts : $2 \times 10 = 20$
 - (a) If V_m is peak voltage across secondary of a transformer in a bridge full wave rectifier, then peak inverse voltage is given by :
 - (i) V_m
 - (ii) $V_m/2$
 - (iii) $2V_m$
 - (iv) None of them.
 - (b) The Avalanche breakdown in semiconductor diode occurs when :
 - (i) Forward current exceeds a certain value
 - (ii) Reverse bias exceeds a certain value
 - (iii) Forward bias exceeds a certain value
 - (iv) The potential barrier is reached to zero.

- (c) A transistor is operating in active region, under this condition :
- (i) both the junctions are forward bias
 - (ii) both the junctions are reverse bias
 - (iii) Emitter base junction is reverse bias
collector base junction is forward bias
 - (iv) Emitter base junction is forward bias
collector base junction is reverse bias.
- (d) An amplifier circuit of voltage gain 100, 2V output voltage the input voltage applied is
- (e) In enhancement n -channel MOSFET an induces n type channel can be produced between the source and drain if V_{gs} is negative . (True/False)
- (f) Inverting amplifier gain is independent of source resistance. (True/False)
- (g) The output voltage in OPAMP differentiator with input voltage V_i the output voltage is given by when $R = 1K$ and $C = 1\text{pf}$.

- (h) $(CA95.12)_{16} - (9FE.A)_{16} = \dots\dots\dots$
- (i) $A'B'C' + A'B'C + A'BC' + ABC' = \dots\dots\dots$
- (j) The sweep voltage is applied on the axis of CRO.

2. Attempt any four parts : 5×4=20

- (a) Draw the circuit diagram of full wave bridge rectifier and explain the operation and also draw the input and output waveform.
- (b) Determine the currents I_1 , I_2 and I_{D2} for the network shown below (Fig. 1) :

 


Fig. 1

- (c) For the Zener diode network of the Fig. 2, determine V_L , V_R , I_Z and P_Z .

 


Fig. 2

(d) Sketch V_o for the network of Fig. 3 for the input shown :

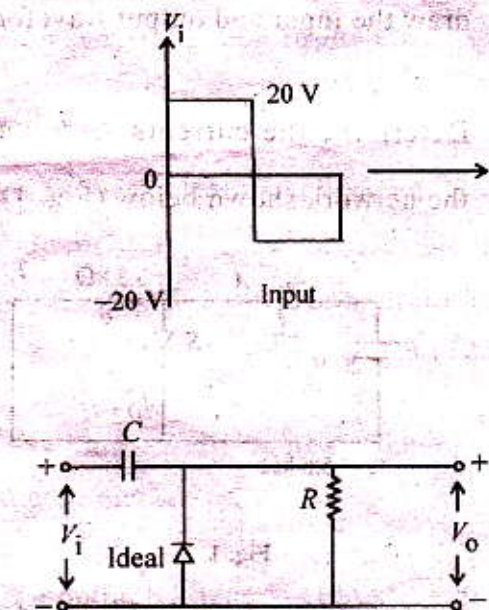


Fig. 3

- (e) Draw the voltage Tripler circuit and explain the operation.
- (f) Determine I , V_1 , V_2 and V_0 for the series of dc configuration in Fig. 4.

 


Fig. 4

3. Attempt any *two* parts : 10×2=20
- (a) Draw the input and output characteristics ($v-i$) of a CE npn transistor configuration with proper levels and discuss how you will determine h_{ie} and h_{fe} hybrid parameters from these characteristics.
- (b) For the voltage-divider bias configuration of Fig. 5 determine (i) I_C (ii) V_E (iii) V_{CC} (iv) V_{CE} (v) V_B (vi) R_1 .

 


Fig. 5

- (c) For the emitter-stabilized bias circuit of Fig. 6, determine (i) I_{B2} (ii) I_{C2} (iii) V_{CE2} (iv) V_C (v) V_B (vi) V_E .

 


Fig. 6

4. Attempt any *two* parts : 10×2=20

(a) What is the significant difference between the construction of an enhancement-type MOSFET and depletion-type MOSFET ? Sketch the basic construction of a *p*-channel depletion-type MOSFET.

(b) Draw a neat schematic diagram of a cathode ray tube with proper labels. How is the intensity of the spot/trace controlled in a cathode ray oscilloscope ?

(c) (i) Sketch a three-input inverting summing circuit and derive an expression for the output voltage.

(ii) Design a non-inverting amplifier circuit that is capable of providing a voltage gain of 15. Assume ideal op-amp and resistances used should not exceed 30 k Ω .

5. Attempt any *four* parts : 5×4=20

(a) Simplify the following function by using the Boolean algebra :

(i)
$$\overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}D + BC\overline{D} + \overline{A}B + B\overline{C}$$

(ii) $(AB + \bar{A}C + BC)(A + \bar{B} + \bar{A}B)$.

(b) Perform the following binary arithmetic operations :

(i) $(1101.1101)_2 - (1001.10)_2$

(ii) $(AB9.54)_{16} + (39C.CD)_{16}$.

(c) Simplify the function using K-map :

$$f(A, B, C, D) =$$

$$\Sigma m(3, 4, 5, 7, 9, 13, 14, 15) + \Sigma d(0, 1, 8, 10)$$

Implement the output using gates.

(d) (i) Convert the given expression into canonical SOP form :

$$f = A + AB + ABC.$$

(ii) Convert the given expression into canonical POS form :

$$f = (A + B)(B + C) + (C + A).$$

(e) What is the universal gate ? Name the universal gate ? Give the proof of universal gate at least for one type of gate.

(f) Draw the block diagram of digital multimeter. Explain the operation of each block.