



Printed Pages : 4

EEEC302

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0323

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech

(SEM III) ODD SEMESTER THEORY EXAMINATION 2009-10
DIGITAL ELECTRONICS

Time : 3 Hours]

[Total Marks : 100

Note : Attempt all questions. Each question carries equal marks.

1 Attempt any four parts :

- Explain the signed binary number representation.
- Given the 8-bit data word 01011011, generate the 13-bit composite word for the Hamming code that corrects single errors and detects double errors.
- Simplify the boolean function in (i) SOP (ii) POS

$$F(x, y, z) = \sum (2, 3, 6, 7)$$

- Simplify the following expression and implement it with two-level NAND gate circuit :

$$Y = BD + BC\bar{D} + A\bar{B}\bar{C}\bar{D}$$

- Simplify the Boolean function f together with don't-care condition using Karnaugh map :

$$F(w, x, y, z) = \sum (1, 3, 4, 13, 15)$$

$$d(w, x, y, z) = \sum (2, 5, 6, 7)$$



- (f) Minimize the following boolean function by using Quine Mc-Clusky method

$$F(A, B, C, D, E) = \sum(20, 28, 37, 39, 48, 56)$$

2 Attempt any **four** parts :

- (a) Design a combinational circuit that adds one to a 4-bit binary number, $A_3A_2A_1A_0$. The circuit can be designed using four half-adders.
- (b) Show that a full-subtractor can be constructed with two-half-subtractors and an OR-gate.
- (c) What do you mean by encoder ? Implement the following functions using 3 : 8 decoder.

$$F_1(A, B, C) = \sum(0, 1, 3, 5, 6)$$

$$F_2(A, B, C) = \sum(0, 2, 4, 7,)$$

- (d) Describe the decimal adder and demultiplexer.
- (e) What is magnitude comparator ? Design a two-bit comparator using logic gates.
- (f) Explain the procedure of binary multiplier.

3 Attempt any **two** parts :

- (a) Differentiate between latches and flip-flop. Draw and explain a master-slave J-K flip-flop.



- (b) Draw the circuit for converting SR flip flop into D flip flop. Also design a one input and one output sequential circuit using D flip flop for the state diagram shown in Fig. 3.1

 


Fig. 3.1

- (c) Design a 4-bit binary synchronous counter with D-flip flop. Also briefly describe the universal shift register.

4 Attempt any two parts :

- (a) Write down the classification of memories. Also draw and explain the programmable logic array.
- (b) What is the difference between flow chart and ASM chart ? Also draw an ASM chart and state table for a 2-bit UP-DOWN counter having mode control input :

M=1 : Up counting M = 0. Down counting. The circuit should generate an output 1 whenever count becomes minimum or maximum.

- (c) Explain the following :
- ROM and PAL
 - Realization of ASM chart using multiplexer.



Attempt any two parts :

- (a) Draw the block diagram of asynchronous segmental circuit and explain its working. Also list the different techniques used for state assignment.
- (b) An asynchronous sequential circuit has two internal states and one output. The excitation functions and output function of the circuit are as follows :

$$Y_1 = \bar{x}_1 x_2 + x_2 y_1$$

$$Y_2 = x_1 y_2 + x_2$$

Output function

$$Z = x_1 + y_2$$

- (i) Derive the logic diagram of the circuit
- (ii) Derive the transition table and output map.
- (c) Define critical race and non-critical race. What is hazard ? Also explain the elimination of Hazard.
-

