

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID: 3073

Roll No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

B. Tech.

(SEM. III) ODD SEMESTER THEORY EXAMINATION

2010-11

SOLID STATE DEVICES AND CIRCUITS

Time : 3 Hours

Total Marks : 100

Note : Attempt all the questions.

1. Answer any four parts : (5×4=20)
 - (a) What is tunnel diode ? Explain its construction with neat and clean figure.
 - (b) What is photo diode ? Explain its construction, operation and characteristics.
 - (c) How Varactor diode works as a voltage variable capacitance ?
 - (d) Describe the V-I characteristics of Schottky diode and give its advantages.
 - (e) What is the responsivity of an InGaAs photodiode if its quantum efficiency is equal to 70% ? The energy gap of InGaAs is 0.75 eV.
 - (f) Explain how a transistor is used as an amplifier.
2. Answer any four parts : (5×4=20)
 - (a) Draw the O/P characteristics of JFET and an enhancement type MOSFET.
 - (b) What are the effects of an emitter-by pass capacitor on low frequency response of a multistage amplifier ?
 - (c) Can a depletion type MOSFET operate in enhancement mode ? If yes, why and how, and if no, why ?

- (d) Describe in detail, how a JFET is biased.
- (e) If $V_D = -4$ V and $I_{DSS} = 4$ mA plot g_m versus I_{DSS} for a JFET.
- (f) Compare JFET and MOSFETs.

3. Answer any two parts : (10×2=20)

- (a) Explain the high frequency response of an Amplifier.
- (b) Explain the effect of bypass capacitor in the functioning of common-source amplifier.
- (c) Derive the expression for the low frequency amplifier gain of common-emitter amplifier.

4. Answer any two parts : (10×2=20)

- (a) Obtain the expression of negative feedback amplifier gain in terms of basic gain of amplifier and feedback factor.
- (b) The gain of an amplifier is 140, when negative feedback is introduced it is reduced to 17.5. Find the value of feedback factor.
- (c) Describe the following
 - (i) Series-series feedback amplifier
 - (ii) Shunt-series feedback amplifier.

5. Answer any two parts : (10×2=20)

- (a) Deduce the condition of oscillation and frequency of oscillation of weinbridge oscillator.
- (b) Write notes on the following :
 - (i) RC oscillators
 - (ii) Crystal oscillators
- (c) If $L = 800$ mH, $C = 0.01$ PF, $R = 1000$ Ω and $C_m = 20$ PF are the various values of an ac equivalent circuit of a piezoelectric crystal, determine F_s and F_p of the crystal.