

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0323

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. III) ODD SEMESTER THEORY EXAMINATION 2012-13

DIGITAL ELECTRONICS

Time : 3 Hours

Total Marks : 100

Note : Attempt all questions. All questions carry equal marks.

1. Attempt any **four** parts of the following : **(5×4=20)**
- The solution to the quadratic equation " $x^2 - 11x + 22 = 0$ " are $x = 3$ and $x = 6$. What is the base of the number system used ?
 - Represent the unsigned decimal number 965 and 672 in BCD and then show the steps necessary to find their sum.
 - Convert the following :
 - $(62.7)_8 = ()_{16} = ()_2$
 - $(BC6)_{16} = ()_{10} = ()_2$
 - Represent the decimal number 6 in (i) Excess-3 code, (ii) BCD code, (iii) Gray code, (iv) 8421 code and (v) 2421 codes.
 - Explain with example using four variable map, how don't care conditions are implemented in K-map minimization.
 - Minimize the following function by Tabular method and implement the result using NAND gate only :


$$f(w, x, y, z) = \Sigma m(1, 4, 8, 9, 13, 14, 15) + d(2, 3, 11, 12)$$

2. Attempt any **two** parts of the following : **(10×2=20)**

- (a) Design a combinational circuit that converts a 3-bit Gray code to a 3-bit binary number. Implement the circuit with
- (i) exclusive OR gate
 - (ii) NAND gate only.
- (b) Design a parity generator to generate an odd parity bit for a 4-bit word. Use EX-OR and $\overline{\text{EX-OR}}$ gate.
- (c) Implement the following function with a multiplexer using A, B, C variables to the selection lines :
- $$F(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15).$$

3. Attempt any **two** parts of the following : **(10×2=20)**

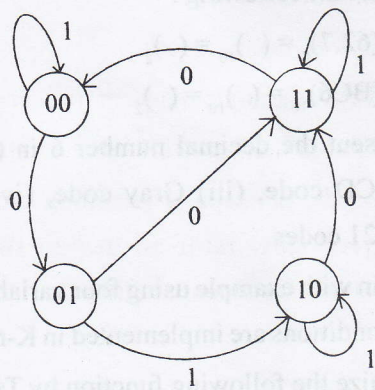- (a) Draw J-K flip flop and write the characteristic table and characteristic equation for it. Explain how will you convert it into T flip-flop.
- (b) Design a clocked sequential circuit for the state diagram.



- (c) Design a 3-bit synchronous counter using J-K flip-flops.

4. Attempt any **two** parts of the following : **(10×2=20)**
- (a) What is RAM ? Distinguish between SRAM and DRAM. Also draw static RAM cell.
 - (b) What is PLA ? Explain the programming table of a PLA. How is the size of a PLA specified ?
 - (c) Explain how a multiplexer can be used as ROM ?

5. Attempt any **two** parts of the following : **(10×2=20)**
- (a) Differentiate between :

- (i) Stable state and unstable state.
- (ii) Critical race and non-critical race.

- (b) An asynchronous sequential circuit has two internal states and one output. The excitation functions and output function of the circuit are as follows :

$$Y_1 = \bar{x}_1 x_2 + x_2 y_1$$

$$Y_2 = x_1 y_2 + x_2$$

and output function

$$Z = x_1 + y_2$$

- (i) Draw the logic diagram of the circuit.
- (ii) Obtain the transition table and output map.
- (c) Discuss the concept of transition table, flow table and primitive flow table to design fundamental mode asynchronous sequential circuit.