

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 0325**

Roll No. 

4	1	0	9	1	2	0	0	5	2
---	---	---	---	---	---	---	---	---	---

**B. Tech.**

**(SEMESTER-III) THEORY EXAMINATION, 2012-13**

**FUNDAMENTALS OF NETWORK ANALYSIS AND SYNTHESIS**


*Time : 3 Hours ]*

*[ Total Marks : 100*



1. Attempt all parts.

10 × 2 = 20

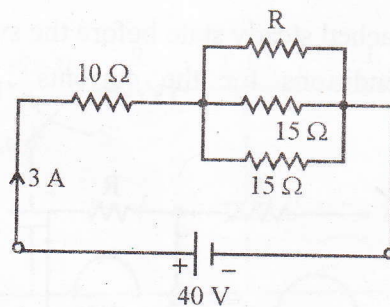
- (a) Draw the line spectra for the signal  $S(t) = 3 \sin\left(t + \frac{\pi}{4}\right)$ .
- (b) Define frequency transformation and frequency normalization.
- (c) Draw the even and odd signal functions for the unit-step function.
- (d) In the below figure, calculate the value of R.



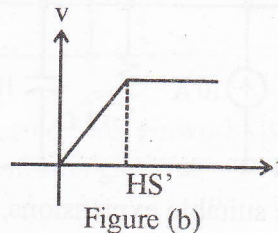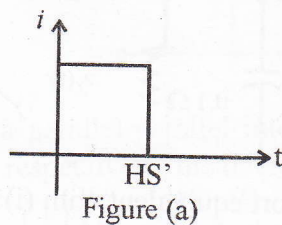
- (e) Two capacitors of  $1 \mu\text{F}$  and  $2 \mu\text{F}$  and connected in parallel across a 25 V dc battery. After the capacitors have been charged, calculate the charge across the two capacitors.
- (f) The current wave shape shown in figure (a) is applied to a circuit element. The voltage across the element is shown in figure (b). Find the type of element used.



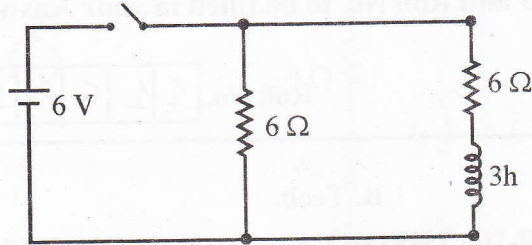- (g) In figure below, the switch is closed at  $t = 0$ . At  $t = 0^+$ , calculate the value of current supplied by battery.



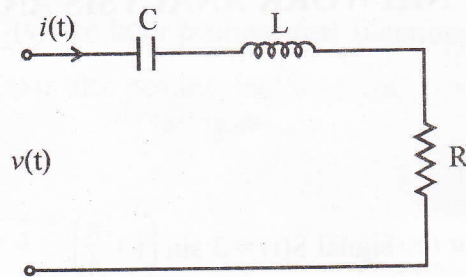- (h) For the figure below, calculate the ratio  $V(s) / I(s)$ .




- (i) List the three properties to recognize an R-C impedance in synthesis.  
 (j) Enlist the two important properties of positive real functions.


2. Attempt any **three** parts :

$3 \times 10 = 30$

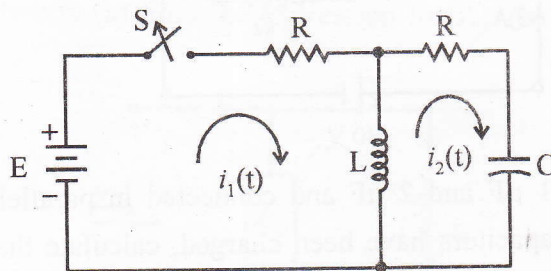- (a) The network shown has reached steady state before the switch S is opened at  $t = 0$ . Determine the initial conditions for the currents  $i_1(t)$  and  $i_2(t)$  and their derivatives.



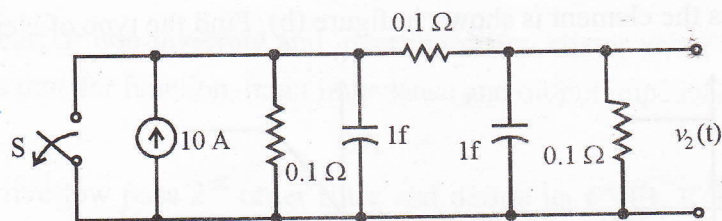- (b) For the circuit shown, the switch S is opened at  $t = 0$ . Use Thevenin's or Norton's theorem to determine the output voltage  $v_2(t)$ . Assume zero initial energy.



- (c) Explain with the suitable expressions, two-port equivalent with (i) one controlled-voltage source and (ii) one controlled-current source.



- (d) Given  $F(s) = \frac{4(S+1)(S+3)}{(S+2)(S+6)}$ , obtain a partial fraction expansion, with all positive residues and hence realize the network in foster form when
- $F(s)$  is an impedance  $z(s)$ .
  - $F(s)$  is an admittance  $y(s)$ .
- (e) (i) Enlist the main properties of a ACTIVE FILTERS.  
(ii) Draw the attenuation characteristics of LPF, BPF, HPF and BRFF.


Answer all the questions :

5 × 10 = 50

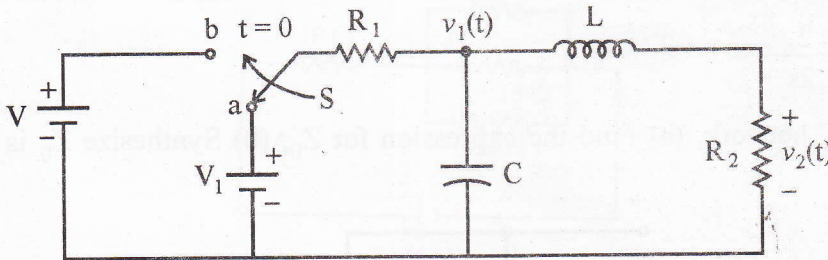
3. (a) The unit-step response of a linear system is  
 $x(t) = (2e^{-2t} - 1) u(t)$
- Find the response  $r(t)$  to the input  $f(t)$ .
  - Sketch the response. Show all pertinent dimensions.
- (b) For the following driving point functions find their simplest network realizations.
- $z(s) = 3 + 2s + \frac{1}{3s}$
  - $y(s) = 2s + \frac{3s}{s+2}$

OR

The network shown has reached steady-state before the switch moves from a to b. Determine the initial conditions for the voltages  $V_1(t)$  and  $V_2(t)$  and their first derivatives.



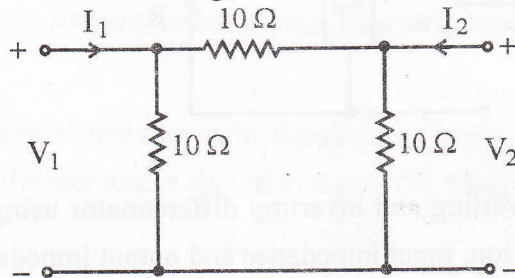4. For the two-port network shown in figure below, determine the admittance matrix.




OR

Prove that in a parallel-parallel interconnected two networks with admittance matrix  $[Y_A]$  and  $[Y_B]$  respectively, the overall y-matrix is given as

$$[Y] = [Y_A] + [Y_B]$$

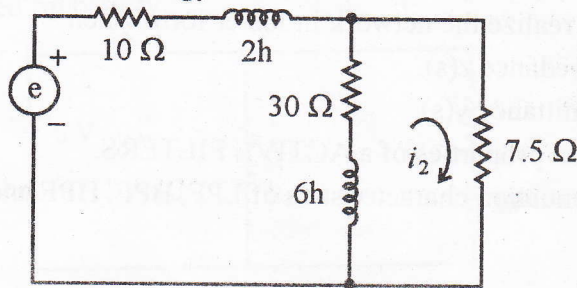5. In figure below, find  $i_2(t)$  using Thevenin's theorem. The excitation is  $e(t) = 100 \cos 20 u(t)$ . Assume zero initial energy.



OR

Suppose  $F_1(s)$  and  $F_2(s)$  are both positive real functions. Discuss the conditions such that  $F(s) = F_1(s) - F_2(s)$  is also positive real function.

6. Given  $z(s) = \frac{s^2 + xs}{s^2 + 5s + 4}$


- What are the restrictions on  $X$  for  $Z(s)$  to be a positive real function?
- Find  $X$  for  $\text{Re}[Z(j\omega)]$  to have a second order zero at  $\omega = 0$ .
- Choose a numerical value for  $X$  and synthesize  $Z(s)$ .

OR

The input impedance for the network shown is

$$Z_{in} = \frac{2s^2 + 2}{s^3 + 2s^2 + 2s + 2}$$

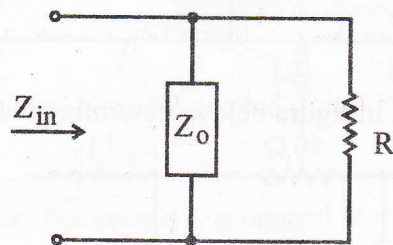If  $Z_0$  is an L-C network, (a) Find the expression for  $Z_0$ , (b) Synthesize  $Z_0$  in a Foster series form.



7. Draw the circuit of non-inverting and inverting differentiator using ideal Op-Amp and determine its transfer function, input impedance and output impedance.

OR

Design an active low pass 2<sup>nd</sup> order filter and define its  $f_{-3dB}$ , Roll-off-rate and also draw its phase response.