

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 131312**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B. Tech.**

(SEM. III) (ODD SEM.) THEORY  
EXAMINATION, 2014-15

**NETWORK ANALYSIS AND SYNTHESIS**

Time : 3 Hours]


[Total Marks : 100

- Note :**
- (1) Attempt All Questions.
  - (2) Assume suitable data if missing.


1 Answer any four parts of the following : **4×5= 20**

- (a) Write the condition for a system to be causal. Is causal system physically realizable or not.
- (b) What do you mean by linear time invariant system? Also differentiate between lumped and distributed elements.
- (c) Write the statement of Norton and Thevenin's theorem. In which type of networks these are not applicable?

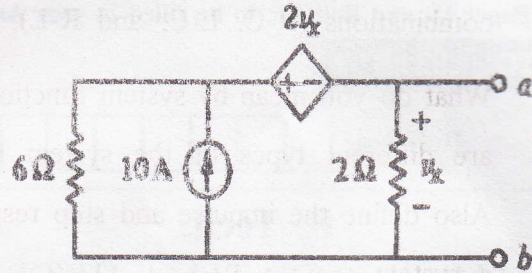- (d) Find the Norton equivalent circuit of the circuit in Figure at terminals a-b.



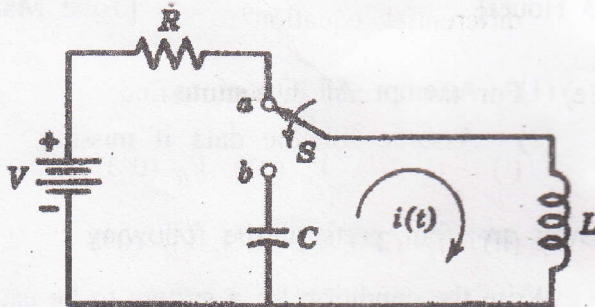- (e) For the network shown, before the switch moves from a to b, steady state conditions prevailed. Find the current  $i(t)$ .




- (f) Prove the convolution theorem and find the convolution of two rectangular pulses of width  $T$  and amplitude  $A$ .


2 Answer any four parts of the following :  $4 \times 5 = 20$

- (a) Write the properties of L-C driving point functions.

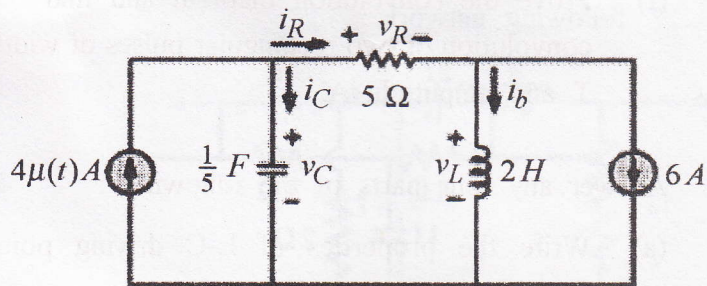- (b) Prove that poles and zeros of driving point functions must be interlace for any one of the combinations (R-C, L-C, and R-L).
- (c) What do you mean by system function? What are different types of the system function? Also define the impulse and step response of a system.
- (d) What do you mean by complementary function and particular integral in the solution of a differential equation?
- (e) For the circuit in Figure find:
- $i_L(0^+)$ ,  $V_c(0^+)$ ,  $V_R(0^+)$
  - $i_L'(0^+)$ ,  $V_c'(0^+)$ ,  $V_R'(0^+)$
  - $i_L(\infty)$ ,  $V_c(\infty)$ ,  $V_R(\infty)$



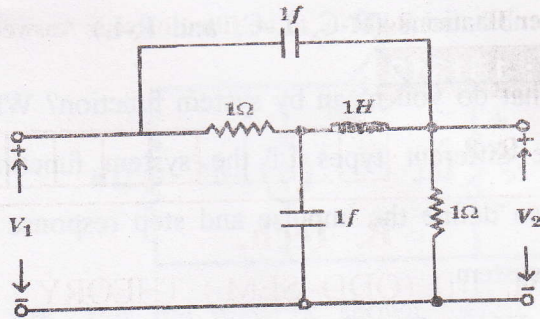(f) Obtain  $\frac{V_2(s)}{V_1(s)}$  for the network shown.




3 Answer any two parts of the following :  $2 \times 10 = 20$

(a) What do you mean by positive real function? Why a driving point function should be positive real to be realizable? Find the conditions of a, b and c such that the following function is positive real function.

$$F(s) = \frac{S^2 + a_1S + a_0}{S^2 + b_1S + b_0}$$

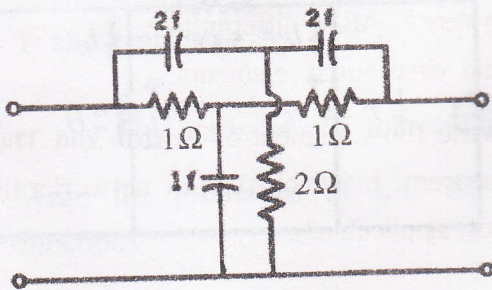(b) Why Y- parameters are called short circuit parameters? Find the Y- parameter of the following network.




131312]

4


[ Contd...

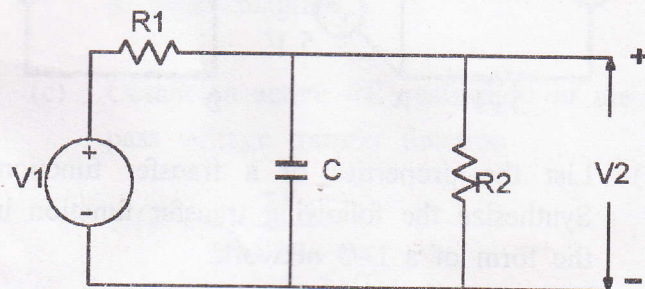- (c) In the given network  $v_1 = e^{-t}$  for  $t \geq 0$  and is zero for all  $t < 0$  if the capacitor is initially uncharged, find the value of  $\frac{d^2 v_2}{dt^2}$  and  $\frac{d^3 v_2}{dt^3}$  at  $t = 0^+$ , Let  $R_1 = 10\Omega$ ,  $R_2 = 20\Omega$  and  $C = \frac{1}{20} F$ .



4 Answer any two parts of the following :  $2 \times 10 = 20$

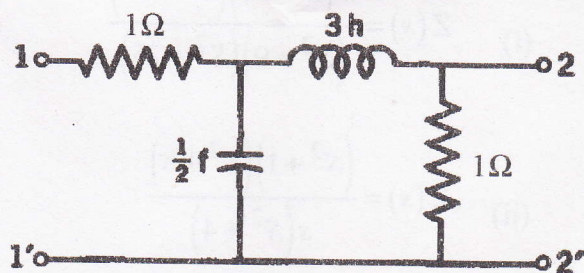- (a) What do you mean by residue condition in terms of transfer function? Show that the residue condition holds for the following network.




131312]

5

[ Contd...

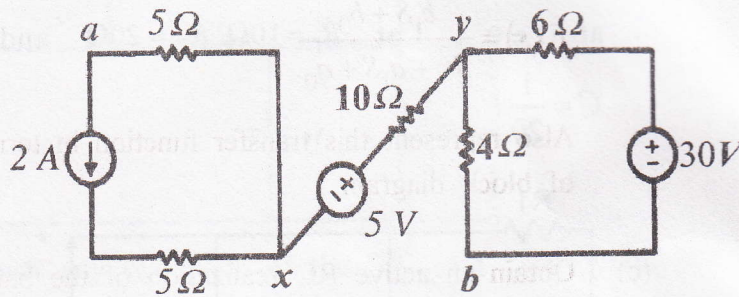- (b) Discuss the properties of R-C driving point impedance function and R-L driving point impedance function. Find the voltage between nodes a and b.



- (c) List the properties of a transfer function. Synthesize the following transfer function in the form of a L-C network.

$$Z(s) = \frac{s^3}{s^3 + 3s^2 + 4s + 2}$$

5 Answer any two parts of the following :  $2 \times 10 = 20$

- (1) Which of the following functions are L-C driving point impedances?

(i) 
$$Z(s) = \frac{s(s^2 + 4)(s^2 + 16)}{(s^2 + 9)(s^2 + 25)}$$

(ii) 
$$Z(s) = \frac{(s^2 + 1)(s^2 + 8)}{s(s^2 + 4)}$$

Also Synthesis the network.

- (b) Discuss briefly the active network synthesis. Determine the damped natural frequency, damping ratio and dc gain of the following transfer function.

$$F(s) = \frac{b_1s + b_0}{s^2 + a_1s + a_0}$$

Also represent this transfer function in terms of block diagram.

- (c) Obtain an active RC realization of the band pass voltage transfer function

$$Z(s) = \frac{2s}{s^2 + 3s + 4}$$

---