

(Following Paper ID and Roll No. to be filled in your Answer Book)

Paper ID : 131301

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--

B. TECH.

(SEM. III) THEORY EXAMINATION, 2015-16

NETWORK ANALYSIS AND SYNTHESIS

[Time:3 hours]

[Total Marks:100]

Section-A

1. Attempt **all** parts. All parts carry equal marks. Write answer of each part in short : (2x10=20)
- Describe the various elements of a network.
 - Write the properties of LC driving point function.
 - What is positive real function ?
 - Write the statement of Thevenin's theorem.
 - Write mathematical expression of 'Unit Step' and 'Unit Impulse' signal used in network analysis.
 - Define 'Transfer function' of a network.

- (g) What do you mean by complex frequency ?
- (h) What is Hurwitz Polynomial ?
- (i) Explain 'zeros of transmission' in a network.
- (j) What do you mean by cut-off frequency of an active filter ?

Section-B

Note: Attempt **any five** questions from this section :

(10x5=50)

2. Prove that in a parallel-parallel interconnected two networks with admittance matrix $[Y_A]$ and $[Y_B]$ respectively. The overall Y-matrix is given by :

$$[Y] = [Y_A] + [Y_B]$$

3. An impedance function is given by :

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

Find the Foster-I and Cauer-I forms for the network.

4. The network shown in the Fig.1 is a current controlled current source. For this network, find the Y parameters.

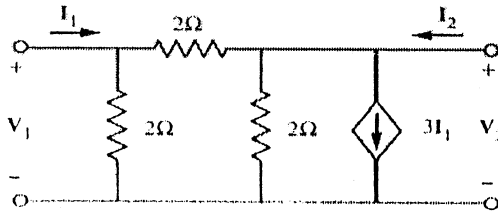


Figure.1

5. In the network shown in Fig.2 $C_1 = C_2 = 1F$ and $R_1 = R_2 = 1\Omega$. The capacitor C_1 is charged to $V_0 = 1V$ and connected across the $R_1 - R_2 - C_2$ network at $t = 0$. C_2 is initially uncharged. Find an expression for $V_2(t)$

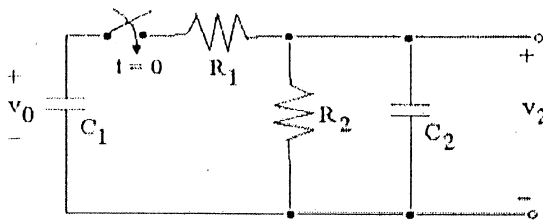


Figure.2

6. Enlist properties of Hurwitz polynomials and positive functions.

7. List properties of transfer function. Determine the circuit elements of the constant resistance bridged-T circuit, shown in Fig.3 that provides the voltage ratio :

$$\frac{V_2(s)}{V_1(s)} = \frac{s^2 + 1}{s^2 + 2s + 1} \text{, Assume } R = 1\Omega$$

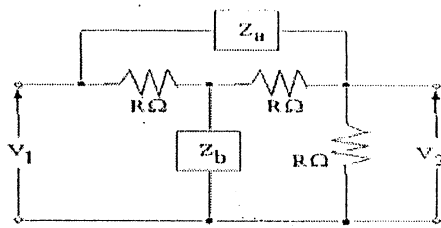


Figure.3

8. Distinguish between Chebyshev approximation and maximally flat approximation as applicable to low pass filters. What is the purpose of magnitude and frequency scaling in low pass filter design ?
9. A third order-Butterworth polynomial approximation is desired for designing a low-pass filter. Determine $H(s)$ and plot its poles. Assume unity d-c gain constant.

Section-C

Attempt **any two** questions from this section.

(15x2=30)

10. The network shown in Fig.4, find $\frac{V_2}{V_1}$ if $Z_a * Z_b = R$

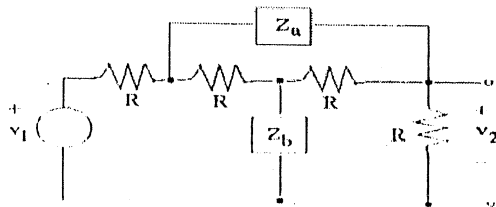


Figure.4

11. Test whether :

- (a) The polynomial $F1(s) = s^4 + s^3 + 2s^2 + 3s + 2$ is Hurwitz; and
- (b) The function $F(s) = \frac{Ks}{S^2 + a}$ is positive real, where a and K are positive constants.

12. Realize the impedance $z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$ in any

three forms of synthesis given below :

- (a) Foster-I form
- (b) Foster-II form
- (c) Cauer-I form
- (d) Cauer-II form

—x—