

B. Tech
SEM III THEORY EXAMINATION 2017-18
DIGITAL LOGIC DESIGN

Time -3.00 hr

Total Marks : 70

Note: 1. Attempt all sections. If require any missing data; then choose suitably.

SECTION – A

1. Attempt all questions in brief.

2 x 7 = 14

- (a) Write four advantages of Digital Systems over Analog Systems.
- (b) Write the Excitation table and characteristic equation of JK flip flop
- (c) Write the difference between combinational and sequential circuits.
- (d) What is $(33)_6 + (45)_6$
- (e) Implement the Expression $Y = ABC' + BD + E$ using Nand gate only.
- (f) Convert the following
 - (i) $(562.13)_7 = (?)_{10}$
 - (ii) $(467.342)_8 = (?)_{10}$
- (g) What is race around condition?

SECTION – B

2. Attempt any three of the following:

7 x 3 = 21

- (a) Simplify the following Boolean function using K-map
 $Y = \sum m(0,1,3,5,6,7,9,11,16,18,19,20,21,22,24,26)$
- (b) Write the steps for combinational circuit designing and design a circuit of three input which gives an high output whenever the sum of LSB & MSB bit is 1.
- (c) Implement the function $F = \sum m(0,1,3,4,7,8,9,11,14,15)$ using 8:1 mux
- (d) Draw and explain the PISO, PIPO register.
- (e) Draw and explain 4-bit by 3-bit multiplier

SECTION – C

3. Attempt any one part of the following:

7 x 1 = 7

- (a) Design a universal shift register that performs HOLD, SHIFT RIGHT, SHIFT LEFT, & LOAD
- (b) Generate the hamming code for the word 11011. Assume that a single error occurs while storing the generated hamming code. Explain how this single error is detected.

4. Attempt any one part of the following:

7 x 1 = 7

- (a) Draw and explain 4-bit magnitude comparator
- (b) Draw a decimal adder to add BCD numbers.

5. Attempt any one part of the following:

7 x 1 = 7

- (a) Draw and explain the operation of a RTL NOR gate

(b) Draw and explain the operation of a TTL NAND gate.

6. Attempt any one part of the following:

7 x 1 = 7

(a) An asynchronous sequential logic circuit is described by the following excitation and output function

$$y = X_1X_2 + (X_1 + X_2)Y$$

$$Z = y$$

Draw the logic diagram of the circuit, Also derive the transition table and output map.

(b) Design a 3 bit up/down ripple counter

7. Attempt any one part of the following:

7 x 1 = 7

(a) Write short notes on RAM and PLA

(b) Derive the state table and state diagram of the synchronous sequential circuit shown below (X is an input to the circuit). Explain the circuit function.

