

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 0321**Roll No. 

--	--	--	--	--	--	--	--	--	--

**B.Tech.**

(SEM IV) EVEN SEMESTER THEORY EXAMINATION, 2009-2010

**ELECTRONIC CIRCUITS**


Time : 3 Hours

Total Marks : 100


Note : Attempt *all* questions.

1. Attempt any four parts of the following :

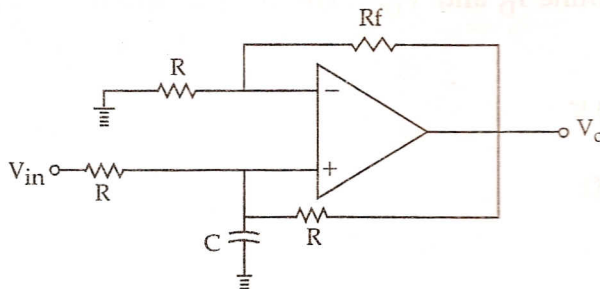- (a) Derive a relationship between input and output voltages for the circuit shown in following figure




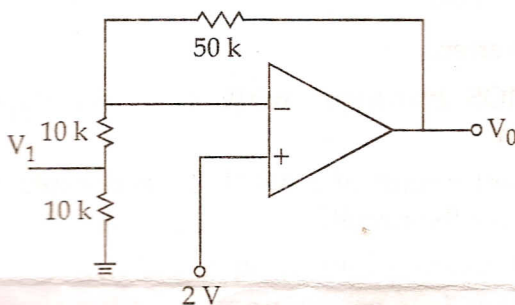- (b) Obtain the voltages
- $V_1$
- and
- $V_0$
- in following figure.



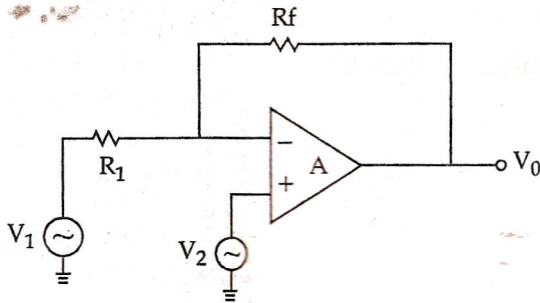- (c) Describe how the performance of an Op-amp is affected by the open loop gain of amplifier ?
- (d) Show that the output voltage of following circuit is :


$$V_0 = \left( \frac{R_f}{R_1} \right) (V_2 - V_1) + V_2$$



- (e) Draw the circuit diagram of a difference amplifier and explain its working.
- (f) Describe the difference between inverting and non-inverting op-amp.

2. Attempt any four of the following :


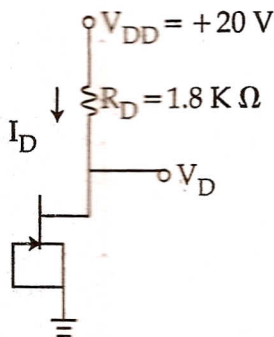
- (a) Analyze the circuit to determine  $I_D$  and  $V_D$ . The JFET is specified to have  $V_p = -4V$  and  $I_{DSS} = 10 \text{ mA}$ .




- (b) Explain the working of MOSFET inverter.
- (c) Obtain ON resistance of an NMOS transistor with  $V_{GS} = 3V$ ,  $V_{th} = 1V$ ,  $\mu_n c_{ox} = 25 \text{ mA/V}^2$ ,  $W = 3 \mu\text{m}$ ,  $L = 1 \mu\text{m}$ .
- (d) Draw the high frequency equivalent circuit of a MOSFET and explain the significance of the different elements of the circuit.
- (e) Explain operation of a MOSFET and explain its use as an amplifier.
- (f) Draw and explain the frequency response of CS-amplifier.

3. Attempt any two of the following :

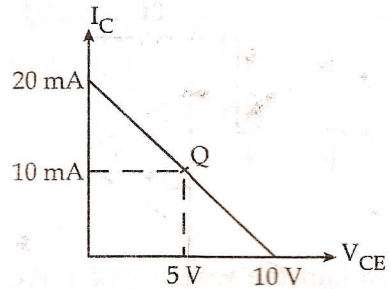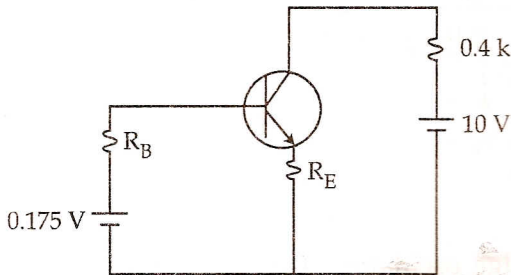- (a) Why transistor action can not be achieved by connecting two diodes back to back. Discuss briefly the charge transport mechanism in a BJT.
- (b) Calculate  $R_E$ ,  $R_B$  and  $\Delta I_{CQ}$  if  $40 < B < 120$  of a silicon transistor with  $I_{CQ} = 10\text{mA}$ ,  $V_{CQ} = 5\text{V}$  of following fig :



- (c) Obtain the 3.db frequency and draw its voltage gain plot.

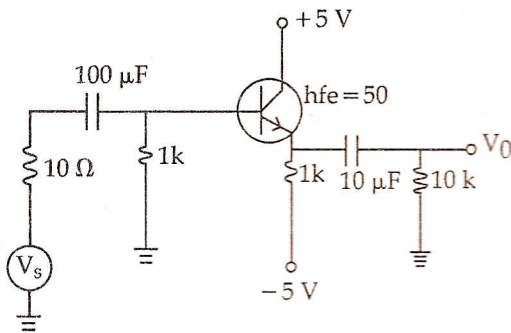

4. Attempt any two of the following :


- (a) Draw the circuit diagram of a CS differential amplifier and derive the expression for its voltage gain.
- (b) Explain the small-signal operation of the BJT differential amplifier and hence show that the differential input resistance  $R_{id}$  is given as :

$$R_{id} = (\beta + 1) (2r_e + 2R_E)$$

- (c) Explain the working of differential amplifier with active load.

5. Attempt any two of the following :

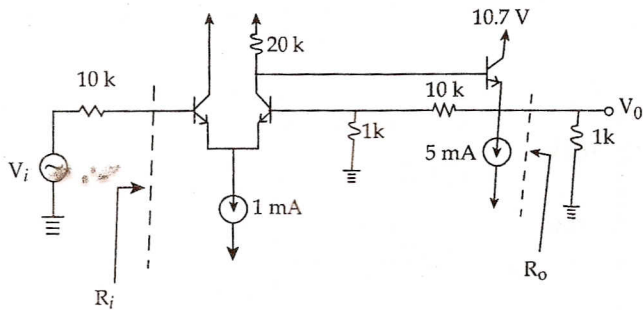- (a) Explain the effect of negative feedback on (i) gain and stability (ii) distortion of an amplifier.
- (b) Obtain  $A_v$ ,  $\beta$ ,  $A_{vf}$ ,  $R_i$ ,  $R_{if}$ ,  $R_o$  and  $R_{of}$  of following circuit.



- (c) Explain the working of a Weinbridge oscillator. Derive an expression for the frequency of oscillations. What are the merits and demerits of such oscillator ?