

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0321

Roll No.

--	--	--	--	--	--	--	--	--	--

**B. Tech.**

(SEM. IV) THEORY EXAMINATION 2010-11

**ELECTRONIC CIRCUITS**

Time : 3 Hours

Total Marks : 100

Note :- (1) Attempt *all* questions.

(2) All questions carry equal marks.

1. Attempt any **FOUR** parts of the following :— (4×5)
  - (a) Draw the circuit of difference amplifier using OP-AMP and apply superposition to determine the common mode gain expression.
  - (b) Draw the circuit diagram of inverting weighted summer calculate the output voltage for the same.
  - (c) Derive the expression for closed loop gain of non-inverting configuration of OP-AMP. What are its characteristics ? Discuss the effect of finite open loop gain.
  - (d) (i) Using non-inverting input draw the practical circuits of
    - (i) VCVS
    - (ii) CCVS
  - (ii) An OP-AMP having 106dB gain at dc and a single pole frequency response with  $f_1 = 2$  MHz is used to design a non-inverting amplifier with nominal dc gain of 100.

Find the 3dB frequency of the closed loop gain.

(e) Define :—

- (i) Slew rate
- (ii) Half power bandwidth.


An OP-AMP has a rated output voltage of  $\pm 10V$  and slew rate of  $1 V/\mu S$ . What is the Half power bandwidth if an input sinusoid with frequency  $f = 5 f_M$  is applied to a unity gain follower constructed using this OP-AMP. What is the maximum possible amplitude that can be accommodated at output without incurring SR distortion ?

(f) What is "Input Bias current" of an OP-AMP ? How its effect can be reduced by connecting a resistance in the non-inverting terminal explain with mathematical expression.

2. Attempt any **TWO** parts of the following :— (2×10)

- (a) (i) Name the different biasing methods of MOSFET. Describe in detail the biasing using a constant current source. Implement this biasing for the application of current mirror.
- (ii) A MOSFET is to operate at  $I_D = 0.1 \text{ mA}$  and to have  $g_m = 1 \text{ mA/V}$  if  $K'_n = 50 \mu A/V^2$ . Find the required W/L ratio and overdrive voltage.
- (b) Explain the working of common source amplifier with a resistance connected in source lead. Draw its small signal equivalent circuit neglecting  $r_o$  and deduce the expression for overall voltage gain.

- (c) (i) Design the circuit given in Fig. 1 to obtain a current  $I_D$  of  $80 \mu\text{A}$ . Find the value required for  $R$  and find the dc voltage  $V_D$ . Let the NMOS transistor have  $V_t = 0.6 \text{ V}$ ,  $\mu_n \cdot C_{ox} = 2000 \mu\text{A}/\text{V}^2$ ,  $L = 0.8 \mu\text{m}$  and  $W = 4 \mu\text{m}$ . Assume  $\lambda = 0$ .

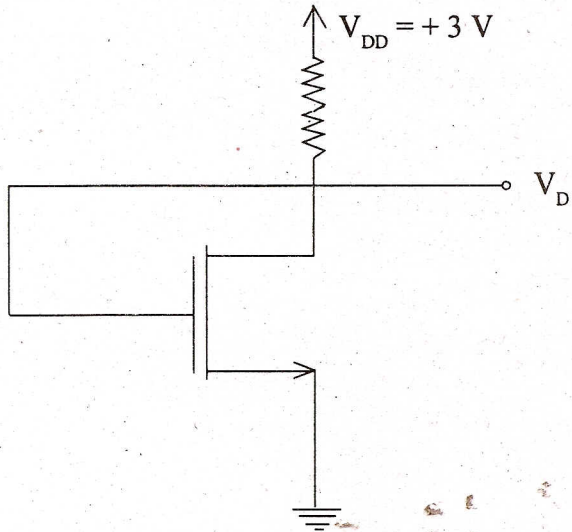

**Fig. 1**

- (ii) Re-design the circuit given in Fig. 1 to double the value of  $I_D$  without changing  $V_D$ . Give and values of  $W/L$  and  $R$ .
3. Attempt any **TWO** parts of the following :— (2×10)
- (a) Draw the circuit diagram of CE amplifier. Replacing the transistor with its hybrid  $\Pi$  model deduce the expression for its voltage gain.
- (b) (i) Discuss the various internal capacitances in detail for BJT.

- (ii) Draw the high frequency hybrid  $\Pi$  model of BJT.  
Derive the expression given below :

$$f_T = \frac{g_m}{2\pi (C_{\Pi} + C_{\mu})}$$

- (c) Write the steps through which small signal equivalent circuit model can be used in the analysis of transistor amplifier.

Analyze the transistor amplifier given in Fig. 2 to determine its voltage gain. Assume  $\beta = 100$ .


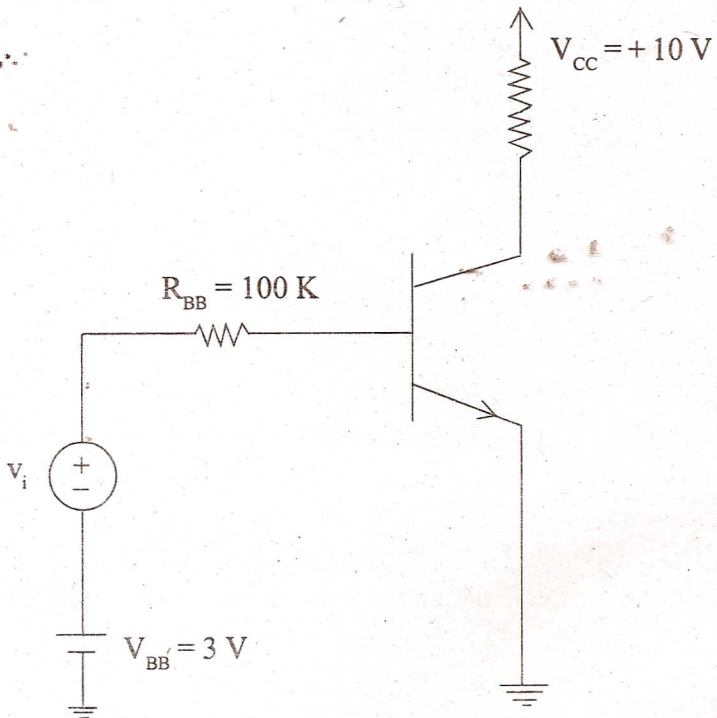


Fig. 2

4. Attempt any **TWO** parts of the following :— (2×10)
- (a) Write the features of differential amplifier. Draw the circuit of MOS differential pair configuration and describe its common mode operation for the determination of over drive voltage.
- (b) For a MOS amplifier with differential input, prove that  $g_m = \frac{I}{V_{OV}}$  where symbols have their usual meaning.
- (c) (i) Explain the advantages of an active load. Draw a circuit of MOS differential amplifier with active load.
- (ii) An N MOS balanced output differential amplifier is operated at a bias tail current of 0.5 mA and has a  $\frac{W}{L}$  ratio of 50,  $\mu_n C_{ox} = 250 \mu A/V^2$  and  $R_D = 4 \text{ k}\Omega$ . Find  $g_m$  and  $A_d$  assume  $\lambda = 0$ .
5. Answer any **FOUR** parts of the following :— (4×5)
- (a) Mention the advantages of negative feedback and discuss its effect on :
- (i) Frequency response and bandwidth expression.
- (ii) Non-linear distortion.
- (b) Explain the working of trans-conductance amplifier using BJT and derive the expression for closed loop trans-conductance.

- (c) For the MOS source follower shown in Fig. 3, calculate the value of  $A_{v_f}$ ,  $R_{i_f}$ ,  $R_{o_f}$  and  $\beta$ .

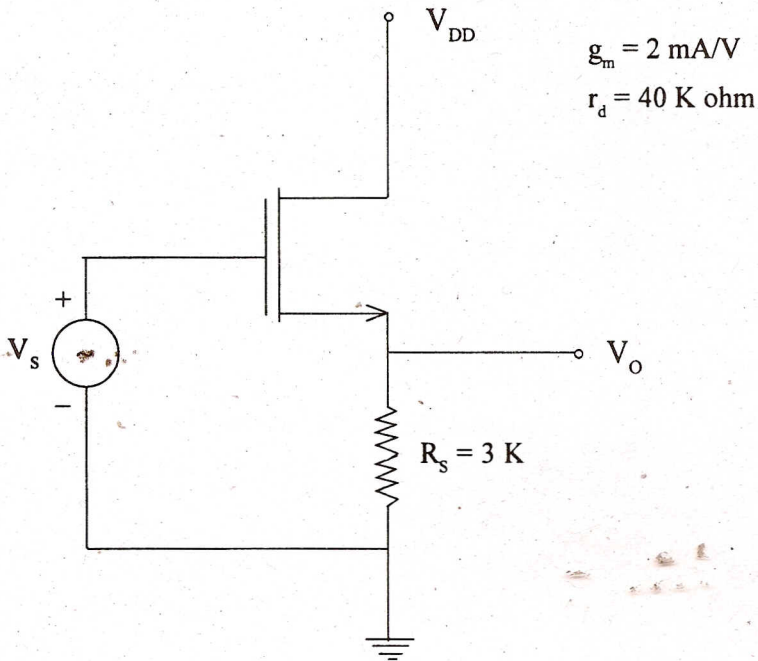

**Fig. 3**

- (d) Write the disadvantages of RC phase shift oscillator. Draw the circuit diagram of RC phase shift oscillator and derive the expression for frequency.

- (e) Draw the circuit of colpitts oscillator using MOSFET devices and show that tank circuit capacitors are in the ratio given as

$$\frac{C_2}{C_1} = g_m R.$$

- (f) What is piezoelectric crystal ? Derive the expression of the ratio of frequency in series and parallel resonance in a piezoelectric crystal.