

6

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 0321**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B.Tech.**  
**(SEMESTER-IV) THEORY EXAMINATION, 2011-12**  
**ELECTRONIC CIRCUITS**

*Time : 3 Hours ]*

*[ Total Marks : 100*

*Note :* Attempt questions from **all** sections. Assume missing data if any.

**Section – A**

1. Answer **all** parts.

**10 × 2 = 20**

- (a) What is the minimum number of terminals required by a single Op-Amp ? What is the minimum number of terminals required on an integrated-circuit package containing four Op-Amps ?
- (b) Design a simple current divider that will reduce the current provided to a  $1\text{ K}\Omega$  load to 20% of that available from the source.
- (c) Design an inverting closed loop amplifier having a gain of  $-10$  and an input resistance of  $100\text{ K}\Omega$ . Calculate values of  $R_1$  and  $R_2$ .
- (d) Define full-power band-width in an Op-Amp.
- (e) For NMOS transistor, write the drain current expression in Triode region and Saturation region.
- (f) Draw a large-signal equivalent circuit model of the n-channel MOSFET in saturation, incorporating the output resistance.
- (g) Calculate  $\beta$  for two transistors for which  $\alpha = 0.99$  and  $0.98$ .
- (h) A BJT having  $\beta = 100$  is biased at a dc collector current of  $1\text{ mA}$ . Find the value of  $g_m$  and  $r_e$ .
- (i) Define the input common – mode range of a Differential Amplifier.
- (j) Define Transconductance and Trans-resistance Amplifiers.

**Section – B**

2. Attempt any **three** parts :

**3 × 10 = 30**

- (a) (i) Consider the basic differential amplifier circuit with  $R_1 = R_3 = 2 \text{ k}\Omega$  and  $R_2 = R_4 = 200 \text{ k}\Omega$ . Find the value of  $A_d$ ,  $R_{id}$ , and  $R_o$ .
- (ii) An Op-Amp having a slew-rate of  $20 \text{ V}/\mu\text{s}$  is to be used in the unity-gain follower configuration, with input pulse that rises from 0 to 3V. What is the shortest pulse that can be used while ensuring full-amplitude output ?
- (b) A transistor amplifier is fed with a signal source having an open-circuit voltage  $v_{sig}$  of 10 mV and internal resistance  $R_{sig}$  of 100 k $\Omega$ . The voltage  $v_i$  at the amplifier input and output voltage  $v_o$  are measured both without and with load resistance  $R_L = 10 \text{ k}\Omega$  connected to the amplifier output. The measured results are as follows :

	v <sub>i</sub> (mV)	v <sub>o</sub> (mV)
Without R <sub>L</sub>	9	90
With R <sub>L</sub> connected	8	70

Find all the amplifier parameters.

- (c) Draw the circuit diagram of single stage CE amplifier, implement hybrid- $\pi$  model and T-model for it and calculate expressions for  $i_e$ ,  $g_m$  and  $i_b$ .
- (d) Draw the NMOS differential amplifier with a common-mode input signal and calculate the Common Mode Gain and CMRR. Also explain the effect of  $R_D$  mismatch on CMRR.
- (e) Design a series – series feedback amplifier and calculate expressions for  $A_p$ ,  $R_{of}$  and  $R_{if}$ .

**Section – C**

Attempt **all** parts.

**5 × 10 = 50**

3. Attempt any **two** parts.

- (a) A MOSFET is to operate at  $I_D = 0.1 \text{ mA}$  and is to have  $g_m = 1 \text{ mA/V}$ . If  $k_n = 50 \mu\text{A/V}^2$ , find the required W/L ratio and the overdrive voltage.
- (b) Draw the high-frequency equivalent circuit model for the MOSFET and list all MOSFET internal capacitances.
- (c) For the CS amplifier, determine its low frequency transfer function.

4. Attempt any **two** parts.
- Draw the circuit diagram of biasing the MOSFET using a constant-current source and calculate the expression for  $I$  in terms of  $I_{REF}$ .
  - Discuss the various internal capacitances in detail for BJT.
  - Draw the circuit diagram of CB amplifier and calculate expression for short-circuit current gain with T-model.
5. Attempt any **two** parts.
- Consider a CE circuit using a BJT having  $I_S = 10^{-15} \text{ A}$ , a collector resistance  $R_C = 6.8 \text{ k}\Omega$ , and a power supply  $V_{CC} = 10 \text{ V}$ .
    - Determine the value of the bias voltage  $V_{BE}$  required to operate the transistor at  $V_{CE} = 3.2 \text{ V}$ . What is the corresponding value of  $I_C$ ?
    - Find the voltage gain  $A_V$  at this bias point.
  - Explain how to operate the BJT as a switch.
  - Calculate the  $R_{in}$  or  $R_{out}$  for the CC amplifier.
6. Attempt any **two** parts.
- Draw the circuit diagram of BJT differential pair and explain its large-signal operation.
  - Calculate the transconductance  $G_m$  for the active-loaded MOS differential pair.
  - For the active-loaded BJT differential amplifier let  $I = 0.8 \text{ mA}$ ,  $V_A = 100 \text{ mV}$  and  $\beta = 100$  find  $G_m$  &  $R_o$ .
7. Attempt any **two** parts.
- Explain how Negative feedback affects Gain, Band-width & Noise.
  - Draw the circuit diagram of a Wien-bridge oscillator and derive an expression for the frequency of oscillations.
  - For the Hartley Oscillator, derive an expression for the frequency of oscillation.