

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 130401 Roll No. 

1	2	0	3	2	3	1	1	2	5
---	---	---	---	---	---	---	---	---	---

**B.Tech.**

(SEM. IV) THEORY EXAMINATION 2013-14

**ELECTRONICS CIRCUITS**

Time : 3 Hours

Total Marks : 100

Note :- Attempt all Sections.

**SECTION-A**

1. Attempt all parts : (10×2=20)
- (a) Explain the basic current mirror with suitable diagram.
  - (b) Explain the properties of Negative Feedback.
  - (c) Define the Barkhausen criteria for oscillators.
  - (d) Define the pinch-off and threshold voltage of MOSFET.
  - (e) Calculate  $\beta$  and  $\alpha$  for a transistor if emitter current is 10 mA and collector current is 9 mA.
  - (f) What are AC and DC Coupled Amplifiers ?
  - (g) What are Error Correcting Amplifiers ?
  - (h) Why voltage divider biasing is preferred ?
  - (i) For NOMS transistor, write the drain current expression in Triode region and Saturation region.
  - (j) Define Trans-resistance amplifier.

### SECTION-B

2. Attempt any **three** parts : **(3×10=30)**
- (a) Explain Input and Output characteristics of Bipolar Transistors in case of common emitter.
  - (b) Explain the operation of Depletion-type MOSFET with its current voltage characteristics of MOSFET.
  - (c) Calculate  $A_v$ ,  $R_{if}$  for series-series feedback amplifier.
  - (d) Explain the frequency response of the CE Amplifier.
  - (e) What is emitter stabilization in self-bias circuit of an n-p-n transistor in CE configuration ? Derive the mathematical expressions for stability factors in this.

### SECTION-C


Note :- Attempt all questions.

3. Attempt any **two** parts : **(5×10=50)**
- (a) For the CS amplifier, determine its low frequency transfer function.
  - (b) Explain the four feedback topologies.
  - (c) Draw the high frequency equivalent circuit model for the MOSFET and list all MOSFET Internal Capacitances.



4. Attempt any two parts :

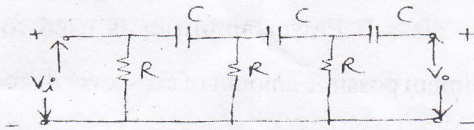- (a) For the given RC phase shift oscillator calculate the frequency of oscillation.




- (b) Explain Piezoelectric type crystal oscillator in detail.  
 (c) Draw the circuit diagram of LC oscillators. What is the condition of oscillation.

5. Attempt any two parts :

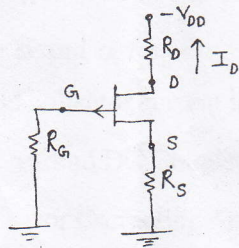- (a) Determine the value of  $R_s$  required to bias a P-channel JFET whose parameters are :

$I_{DSS} = 18 \text{ mA}$ , and  $V_p = -8\text{V}$ . The JFET is used in self bias arrangement shown in figure. Required gate-source voltage is 4V.



- (b) Consider a MOSFET for which  $W = 8\mu\text{m}$ ,  $L = 0.4\mu\text{m}$ ,  $t_{ox} = 8\text{nm}$ ,  $\mu_n = 450 \text{ cm}^2/\text{V}$  and  $V_t = 0.7$ . Find :  $C_{ox}$ ,  $K_n$ .

(c) Draw the circuit diagram of CB amplifier and calculate expression for short-circuit current gain with T-model.

6. Attempt any **two** parts :

(a) How class-B Power amplifier is used for generating minimum possible amount of crossover distortion.

(b) Draw the architecture for the three-stage amplifier. Explain all three-stages in power amplifier.

(c) Explain how Negative feedback affects Gain and Noise.

7. Attempt any **two** parts :

(a) Explain BJT as an amplifier and as a switch.

(b) Explain large signal operation of BJT differential pair.

(c) Compare the characteristics of BJT and MOS Amplifier.