

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3086

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. V) ODD SEMESTER THEORY EXAMINATION
2010-11


ANALOG INTEGRATED CIRCUITS

Time : 3 Hours

Total Marks : 100

Note : Attempt all the questions.

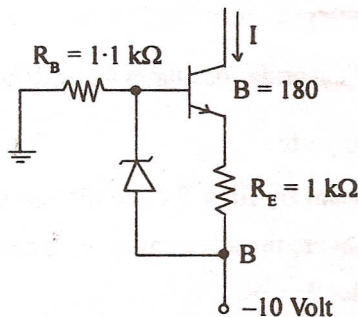
1. Attempt any four parts : (5×4=20)
- (a) Explain brief view of differential amplifier.
- (b) What is the level translator circuit ? What is its significance in a cascade differential amplifier ?
- (c) Calculate current I in the circuit of figure 1.



- (d) Draw the block diagram of an OP-Amp and describe its various blocks.
- (e) Discuss the operation and significance of a multiple output transistor current mirror.
- (f) What is primary advantage of using an active load.

2. Answer any **four** parts : (5×4=20)

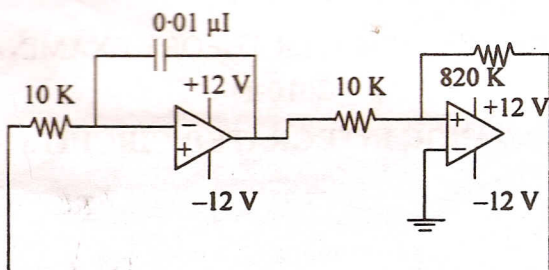- (a) Why timer IC was given the name IC555. What are its essential building blocks ? Explain them.
- (b) Calculate the amplitude of the triangular wave and square wave for fig. (a).




- (c) Explain the difference between capture and lock range of frequencies of the PLL with suitable examples.
- (d) Explain crystal controlled oscillator.
- (e) Determine the frequency and duty cycle for 555 astable multivibrator output for $C = 0.01 \mu\text{F}$, $R_A = 2.2 \text{ k}\Omega$ and $R_B = 3.901 \text{ k}\Omega$.
- (f) Design a Wein bridge oscillator that will oscillate at 2 kHz.


3. Attempt any **two** parts : (10×2=20)

- (a) What is meant by filter ? Give the classification of the filters. What are the advantages of an active filter over a passive filter ?
- (b) Write short notes on any **two** :
- (i) Second order active filter method
 - (ii) High order filters
 - (iii) State variable filter.

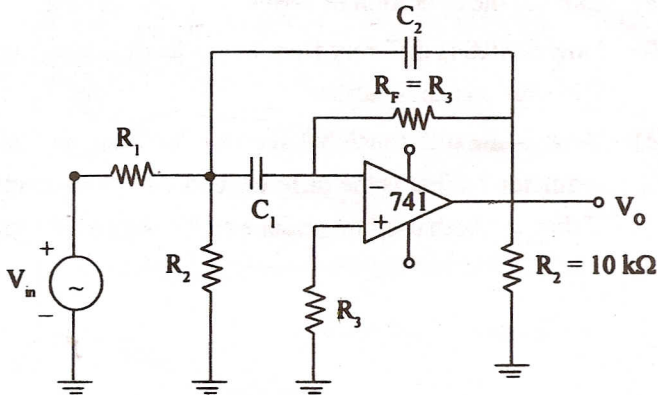- (c) Design a Bandpass filter using the op-amp 741 shown below, so that $F_c = 1 \text{ KHz}$, $Q = 3$ and gain $A_F = 10$.



4. Answer any two parts : (10×2=20)
- Explain the hysteresis loop obtained in the Schmitt trigger operation.
 - Draw a sample-and-hold circuit. Explain its operation briefly.
 - Given a circuit of Fig. which gives square wave output. Find R and C so that square wave with period 10 m secs can be generated.

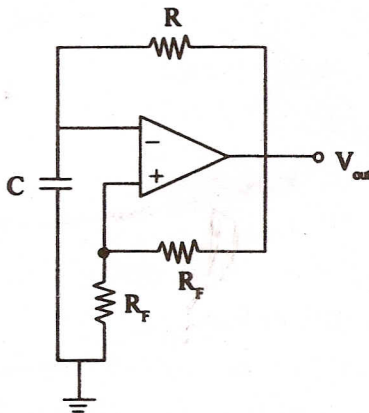

5. Attempt any **two** parts :

(10×2=20)

- (a) Explain the operation of series voltage regulator.
- (b) How SMRS is different from linear feedback regulator ?
Give various applications.
- (c) What is the difference between an 7808 and an 7908 IC regulator ? What is the difference in circuit connections, if they are both used to produce an 8V regulated supply ?