

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2115

Roll No.

--	--	--	--	--	--	--	--	--	--

**B.Tech.**

(SEM. V) THEORY EXAMINATION 2011-12

**ANALOG INTEGRATED ELECTRONICS**

Time : 3 Hours

Total Marks : 100

**Note :-** (1) Attempt all questions.

(2) All questions carry equal marks.

1. Attempt any **two** of the following : **(10×2=20)**
  - (a) Draw the open loop frequency response of operational amplifier (Op-Amp) and explain it.
  - (b) Discuss in brief that how the high frequency model differs from the equivalent circuit of an Op-amp. Discuss frequency response of internally compensated Op-Amp.
  - (c) What is the stability of an Op-amp ? Explain the various stability specifications with constant gain bandwidth product.
  
2. Attempt any **two** of the following : **(10×2=20)**
  - (a) Draw and explain the Instrumentation Amplifier using Op-Amp. Discuss the most desired characteristic of it and maximum limit to that.
  - (b) Design an inverting Op-Amp circuit with a voltage gain of

$A_v = V_o/V_i = -8$ , when the input voltage is  $V_i = -1V$ .

Maximum current in  $R_1$  and  $R_2$  must be no longer than  $15\mu A$ . Determine the minimum values of  $R_1$  and  $R_2$ .

- (c) (i) Draw the I-V converter and derive its output expression.
- (ii) Draw the V-I converter and derive output voltage equation for floating load.

3. Attempt any **two** of the following : **(10×2=20)**

- (a) Design a low pass filter using Op-Amp at a cut-off frequency of 1kHz with pass gain of 2.
- (b) Discuss the classification of active filters and explain its advantage and disadvantage with suitable example using Op-Amp.
- (c) (i) Draw a block diagram and explain the characteristic of successive approximation type A/D converter.
- (ii) For the digital input 1111 with R/2R ladder 4 bit type DAC, find the output voltage and resolution. Assume  $V=10V$  and  $R=10k\Omega$ .

4. Attempt any **two** of the following : **(10×2=20)**

- (a) Write short notes on the following :
- (i) Square wave generator
- (ii) Triangular wave generator.

(b) With the help of a neat block diagram, explain the principle of working of Sample and Hold circuit using Op-Amp. Enlist its applications.

(c) (i) Explain in brief the advantage of Precision rectifier over simple diode rectifier.

(ii) A Precision rectifier having the value of gain is  $-2$  for the negative input and zero otherwise and input resistance is  $100\text{ K}\Omega$  as shown in given figure 1. Determine the value of  $R_1$  and  $R_2$ .

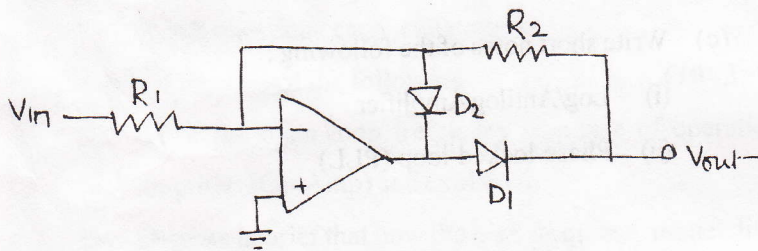



Figure 1

5. Attempt any two of the following :  $(10 \times 2 = 20)$

(a) Using the block diagram explain the functionality of an OTA.

(b) (i) What are the advantages of the adjustable voltage regulator over the fixed voltage regulator ?

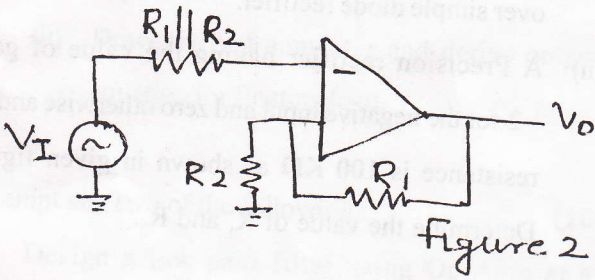- (ii) Determine the value of  $R_1$  and  $R_2$  if the maximum allowable current through them is  $100\mu\text{A}$  for Schmitt Trigger as given in figure 2. Assuming  $V_{\text{sat}} = +10\text{V}$ ,  $-V_{\text{sat}} = -10\text{V}$  and  $V_H = 0.1\text{V}$ .



- (c) Write short notes of the following :

- (i) Log/Antilog Amplifier
- (ii) Phase locked loop (PLL)