

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2117

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEMESTER-V) THEORY EXAMINATION, 2012-13

INTEGRATED CIRCUITS

Time : 3 Hours]

[Total Marks : 100

Section – A

1. Attempt all question parts : **10 × 2 = 20**
- For Widlar Current source assume the $I_{ref} = 1 \text{ mA}$ and $R_2 = 5 \text{ K}\Omega$, neglect base current and find I_{C2} .
 - List the advantages of Widlar current source.
 - Find the voltage gain of the CE amplifier with active load circuit when both devices are active.
 - Define the term “Sensitivity”.
 - Give reason – “The voltage gain of the operational amplifier decreases at high frequencies”.
 - Write some applications of analog multiplier.
 - What are the parameters determine the performance of VCO ?
 - Calculate the time period of Astable Multivibrator having $R_1 = R_2 = 2 \text{ K}\Omega$, $R = 4 \text{ K}\Omega$ and $C = 0.01 \text{ uF}$.
 - Why CMOS NAND is preferred over CMOS NOR ?
 - List the disadvantages of Sallen – Key Unity Gain filter.

Section-B

2. Attempt any three question parts : **10 × 3 = 30**
- Derive a voltage gain expression for Dual Input Balanced Output Differential Amplifier.
 - With neat circuit diagram explain the generation of square wave form using Op-Amp astable multivibrator and calculate its total time period.

(c) Design a Wein-Bridge Oscillator circuit and derive expression for sustained oscillations.

(d) (i) Implement the following expression using AOI gate logic.

$$F = \overline{A(B + CD)}$$

(ii) Explain the transistor sizing procedure for a four input NOR gate.

(e) Design a filter using the Sallen – Key unity gain low pass active filter to meet the following specifications: Assume $C = 0.027 \mu\text{f}$.

(i) Rolloff Rate : 40 dB/decade

(ii) Critical Frequency : 4 kHz

(iii) Pass band as flat as possible

(iv) Gain of 10 at DC

Section – C


Attempt **all** questions :

$10 \times 5 = 50$

3. Attempt any **two** parts :

$5 \times 2 = 10$

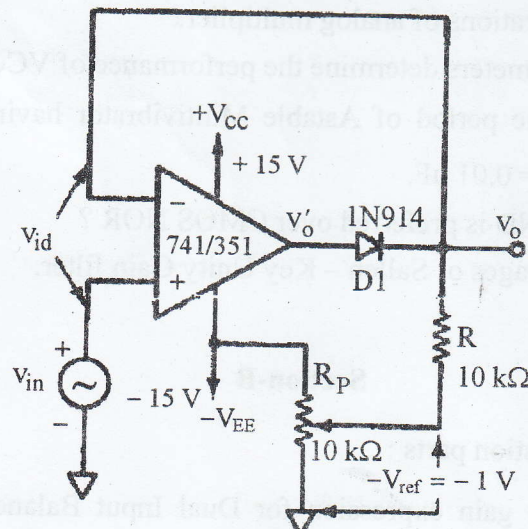(a) Draw the output of the following circuit and explain its working.




(b) Draw a Cascode MOS current mirror and calculate its output impedance.

(c) How Current Mirror can be used as an ACTIVE LOAD ? Draw the BJT differential amplifier circuit using ACTIVE LOAD.

4. Attempt any two parts : 5 × 2 = 10
- (a) What is the effect of V_0 on I_0 in MOS Current Mirrors ?
 - (b) Draw and explain sample and hold Op-Amp circuit.
 - (c) Name the circuit that is used to detect the peak value of the non-sinusoidal waveforms. Explain the operation with neat circuit diagram.

5. Attempt any two parts : 5 × 2 = 10
- (a) Two CMOS inverters operating from a 5-V supply have V_{IH} and V_{IL} of 2.42 V and 2.00 V and corresponding outputs of 0.4 and 4.6, respectively, and are connected as a latch. Approximating the corresponding transfer characteristic of each gate by a straight line between threshold points, sketch the latch open-loop transfer characteristic. What are the coordinates of point B (unstable point) ? What is the loop gain at B ?
 - (b) Draw and explain monostable multivibrator using 555 timer and calculate its time period.
 - (c) (i) Design a precision peak rectifier and explain its working operation.
(ii) Using a 10 nF capacitor, find the value of R that yields an output pulse of 100 μ s in the monostable circuit.

6. Attempt any one part : 10 × 1 = 10
- (a) Draw the KHN Biquad filter and derive transfer function of the BPF and LPF from that.
 - (b) Find the V_{in} / I_{in} for the following circuit :

 

7. Attempt any two parts : 5 × 2 = 10
- (a) Draw and explain the PLL block diagram.
 - (b) Design a parallel-flash ADC and explain its working.
 - (c) Draw and explain a GILBERT analog multiplier.