

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2481

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM. VI) THEORY EXAMINATION 2011-12

ANALOG SIGNAL PROCESSING

Time : 2 Hours


Total Marks : 50

Note :— (1) Attempt all **four** questions.

(2) All questions carry equal marks.

1. Attempt any **two** parts of the following :— **(6×2=12)**

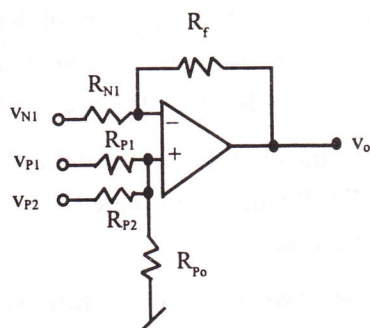- (a) Design a circuit to obtain $v_o = -2v_{N1} + v_{P1} + 2v_{P2}$ in the following configuration. The smallest resistor used should be 10 kΩ.



- (b) Draw the circuit of a non-inverting integrator circuit and find its transfer function.

- (c) Draw the circuit of an inverting-negative half wave rectifier and its transfer characteristics. Explain its working.
2. Attempt any **two** parts of the following :— (6×2=12)
- (a) What is a negative impedance convertor ? Draw its circuit diagram and find the input impedance.
 - (b) Draw the circuit of a capacitance multiplier and find the equivalent circuit of the impedance you obtain.
 - (c) Draw the circuit of a Logarithmic amplifier and use it for the multiplication of two signals. Draw the resulting circuit diagram and find the transfer function.
3. Attempt any **two** parts of the following : (7×2=14)
- (a) Draw the block diagram of Tow Thomas biquad. Derive the circuit diagram of the biquad. Find the transfer function of high pass, low pass functions.
 - (b) Draw the circuit diagram of KHN-biquad. Find the transfer function of band reject, band pass and all pass functions. Also draw the phase plot of all pass function.
 - (c) Draw the circuit of a generalized impedance convertor (GIC). Realize a grounded inductance using GIC and find its value.
4. Attempt any **two** parts of the following :— (6×2=12)
- Write short notes on any **two** of the following :—
- (a) Analog dividers
 - (b) Sallen-key circuits
 - (c) Transconductance cells.