

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 0396

Roll No.

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

**B. Tech.**

(SEM. VIII) THEORY EXAMINATION 2010-11  
**DIGITAL MEASUREMENT TECHNIQUES**

*Time : 3 Hours*

*Total Marks : 100*

**Note :** (1) Attempt all questions.

(2) Marks are indicated at the end of each Section.

1. Attempt any **two** parts of the following : **(10×2=20)**
  - (a) Mention the merits and demerits of digital measurement over analog measurements.
  - (b) Explain with block diagram the working of digital ohmmeter.
  - (c) Explain the working of a digital voltmeter. List different types of DVMs. How can a DVM be used to measure the current ?
  
2. Attempt any **two** parts of the following : **(10×2=20)**
  - (a) Draw the block diagram of digital frequency meter. Explain its principle of operation.
  - (b) Draw the labeled block diagram of :
    - (i) Logic analyzer and
    - (ii) Dual trace Oscilloscope.

- (c) Draw the block diagram of standard signal generator. What features are essential in converting it into square wave and triangular wave generator ?

3. Attempt any two parts of the following : (10×2=20)

(a) Explain how high frequency can be measured by digital techniques.

(b) Discuss in brief the working of Digital programmable amplifier and filters.

(c) Explain the working of a digital multimeter and mention its use.

4. Attempt any two of the following: (10×2=20)

(a) Why Sample and hold circuit is considered as an essential component of modern day's instrumentation system ? Explain the following terms that are associated with the problems of sample-hold circuits : (i) finite aperture time, (ii) signal feed through and (iii) Droop.

(b) Describe in detail the successive approximation method of ADC.

(c) What are the types of DAS ? Mention its applications also. Explain the generalized diagram of a digital data acquisition system.

5. Write short notes on any **four** of the following : (5×4=20)

- (a) R-2R ladder type DAC.
- (b) Indirect type ADC
- (c) Logarithmic A/D Converter
- (d) Decibel meter
- (e) Time Division Multiplexing.