



Roll No:


--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM IV) THEORY EXAMINATION 2024-25
ANALOG CIRCUITS

TIME: 3 HRS**M.MARKS: 100****Note:** Attempt all Sections. In case of any missing data; choose suitably.**SECTION A****1. Attempt all questions in brief.****2 x 10 = 20**

Q No.	Question	CO	Level
a.	Write down the applications of a current mirror circuit.	4	K1
b.	Draw T-model equivalent circuit of NPN transistor.	1	K1
c.	Explain Barkhausen criterion.	3	K2
d.	Explain the principle of crystal oscillator?	3	K1
e.	Define minimum sustainable voltage and maximum usable load of a Current mirror Circuits.	4	K1
f.	Explain the physical significance of CMRR in noisy environment.	5	K1
g.	Define Transconductance Amplifiers.	1	K1
h.	What do you mean by offset voltage of an Op-Amp?	5	K2
i.	Derive the relationship between α and β .	2	K3
j.	A BJT having $\beta = 50$ is biased at a dc collector current of 1 mA. Find the value of g_m and r_e .	2	K3

SECTION B**2. Attempt any three of the following:****10 x 3 = 30**

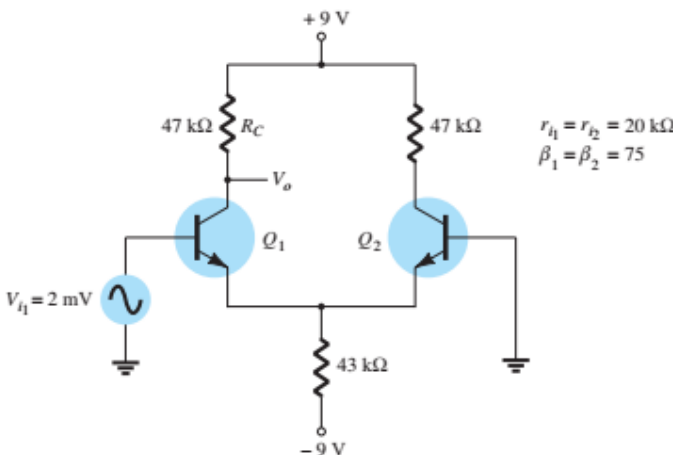Q No.	Question	CO	Level
a.	Draw the circuit diagram of single stage CE amplifier using hybrid- π model and find out the expression of transconductance.	1	K3
b.	Design a shunt-series feedback amplifier and calculate expressions for A_f , R_{of} and R_{if} .	2	K6
c.	Explain the working of Wien Bridge Oscillator. Derive the expression for feedback factor (β) and frequency (f).	3	K3
d.	Calculate the output voltages of the given differential amplifier. 	4	K3
e.	Design the following circuits using op-Amp: i) Logarithmic amplifier ii) Integrator circuit	5	K6



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM IV) THEORY EXAMINATION 2024-25
ANALOG CIRCUITS

TIME: 3 HRS

M.MARKS: 100

SECTION C

3. Attempt any one part of the following: 10 x 1 = 10

Q No.	Question	CO	Level
a.	Draw the circuit diagram of single stage CC amplifier using T-model and find out the expression of voltage gain.	1	K3
b.	Show the effect of multi stage amplification in low and high frequency applications.	1	K6


4. Attempt any one part of the following: 10 x 1 = 10

Q No.	Question	CO	Level
a.	Draw the high frequency model of MOSFET and drive an expression of f_H .	2	K3
b.	Design a series-shunt feedback amplifier and calculate expressions for A_f , R_{of} and R_{if} .	2	K6

5. Attempt any one part of the following: 10 x 1 = 10

Q No.	Question	CO	Level
a.	Draw the circuit of an RC phase shift oscillator using op-amp and derive frequency and condition of oscillation.	3	K3
b.	For the Hartley Oscillator, derive an expression for the frequency of oscillation.	3	K3

6. Attempt any one part of the following: 10 x 1 = 10

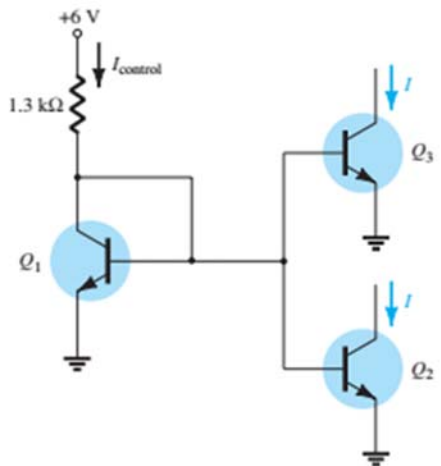Q No.	Question	CO	Level
a.	Draw the basic structure of differential amplifier and calculation the differential gain, common mode gain and CMRR.	4	K3
b.	Calculate the current I through each of the transistor Q_2 and Q_3 in the given circuit. 	4	K3



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM IV) THEORY EXAMINATION 2024-25
ANALOG CIRCUITS


TIME: 3 HRS

M.MARKS: 100

7. Attempt any *one* part of the following:

10 x 1 = 10

Q No.	Question	CO	Level
a.	Explain the effect of finite loop gain and bandwidth on the performance of Op-Amp considering non-inverting configuration.	5	K2
b.	Find out the output voltage (V_o) of the following circuit using ideal Op-Amp.	5	K3

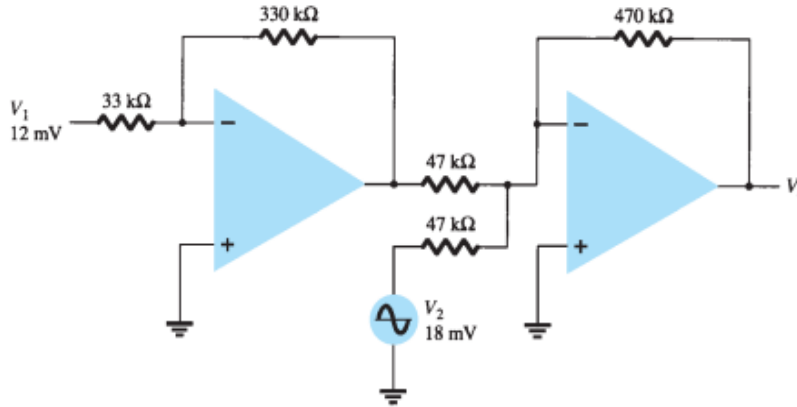

QP25EP1_143 | 24-Jul-2025 1:37:36 PM | 122.185.51.242