

Roll No:


--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM I) THEORY EXAMINATION 2024-25
BASIC ELECTRICAL ENGG

TIME: 3 HRS**M.MARKS: 100****Note:** Attempt all Sections. In case of any missing data; choose suitably.**SECTION A****1. Attempt all questions in brief.****2 x 10 = 20**

Q no.	Question	Marks	CO
a.	What is ideal current source.	2	1
b.	Differentiate between mesh and loop	2	1
c.	Define active power.	2	2
d.	Write the significance of power factor.	2	2
e.	What is eddy current in transformer.	2	3
f.	Define magnetic circuit.	2	3
g.	Classify the DC motor.	2	4
h.	What is the need of starter.	2	4
i.	Define earthing.	2	5
j.	Define fuse.	2	5

SECTION B**2. Attempt any three of the following:****10 x 3 = 20**

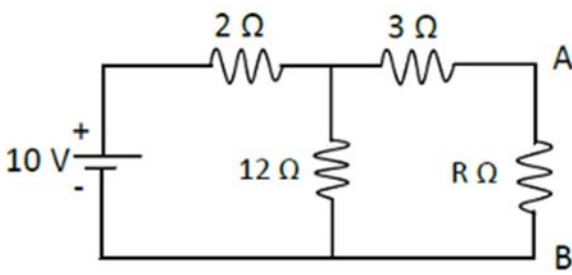Q no.	Question	Marks	CO
a.	Draw the Norton's equivalent circuit for the circuit shown in figure 	10	1
b.	An unbalanced four wire star connected load has a balanced voltage of 400V, the loads are $Z_1=(4+j8)\Omega$, $Z_2=(3+j4)$ and $Z_3=(15+j20)\Omega$. Calculate the (i) Line currents (ii) Currents in the neutral wire and (iii) Total power.	10	2
c.	Explain Construction of Single Phase Transformer With Neat Diagram?	10	3
d.	Discuss about the principle of operation of DC motors.	10	4
e.	What are the main differences between single-core and multi-core cables? Where are each typically used?	10	5

SECTION C**3. Attempt any one part of the following:****10 x 1 = 10**

Q no.	Question	Marks	CO
a.	Find the Thevenin's equivalent for the circuit shown below	10	1



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM I) THEORY EXAMINATION 2024-25
BASIC ELECTRICAL ENGG

TIME: 3 HRS

M.MARKS: 100

b.	Three resistances of values 20Ω , 30Ω and 50Ω are connected in series across 20 V DC supply. Calculate, i) Equivalent resistance of the circuit. ii) Total current from the supply. iii) Voltage drop across each resistor. iv) Power dissipated in each resistor.	10	1

4. Attempt any one part of the following: 10 x 1 = 10

Q no.	Question	Marks	CO
a.	Derive the voltage and current relations in three phase balanced circuits for star connection.	10	2
b.	Explain resonance for series RLC circuit and derive the equation for resonant frequency	10	2

5. Attempt any one part of the following: 10 x 1 = 10

Q no.	Question	Marks	CO
a.	Explain Three Phase Transformer Connection.	3	3
b.	A 125 KVA transformer having primary voltage of 2000 V at 50 Hz has 182 primary and 40 secondary turns. Neglecting losses, Calculate (i)The full load primary and secondary currents.(ii)The no load secondary induced emf (iii)Maximum flux in the core	3	3

6. Attempt any one part of the following: 10 x 1 = 10

Q no.	Question	Marks	CO
a.	Explain equivalent circuit for single phase induction motor.	4	4
b.	Define significance of torque slip characteristics of 3-phase induction motor	4	4

7. Attempt any one part of the following: 10 x 1 = 10

Q no.	Question	Marks	CO
a.	Why is earthing important in electrical systems, particularly in LT switchgear? Describe at least two types of earthing methods.	5	5
b.	Write note on (i) MCCB (ii) ELCB	5	5